

2015 EE214A Design Project

Kankanala, Usha
ukankana@stanford.edu
SUID:06091239

Lenius, Samuel
lenius@stanford.com
SUID:06091240


December 4, 2015

| Specifications | Given Spec | Achieved Spec |
|-----------------------|--------------|----------------|
| Gain | 30k Ω | 34.7k Ω |
| Bandwidth | 90MHz | 93MHz |
| Power | 2.0mW | 1.0mW |
| FOM | 1350 | 3043 |


| Area Breakdown | % Core Area | Area (μm) |
|-----------------------|-------------|------------------------|
| Core Area | 100% | 112 μm^2 |
| VNMOS-bias | 19.6% | 22 μm^2 |
| VP MOS-bias | 10.7% | 12 μm^2 |
| Bias Generator | 73.1% | 82 μm^2 |

1 Design Outline


Our approach to this design was to first develop sizing ratios of the transistors and their DC relationships to V_x , V_y , V_z and V_o . We developed the equations necessary to ‘program’ those voltages and to develop what their reasonable ranges are. Here are some graphs that show the relationships between the output common mode voltage and V_z , and then V_z to V_y given our sizing decisions. We developed a MATLAB program to quickly estimate critical parameters for a given design, to allow easy investigation of parametric variation.

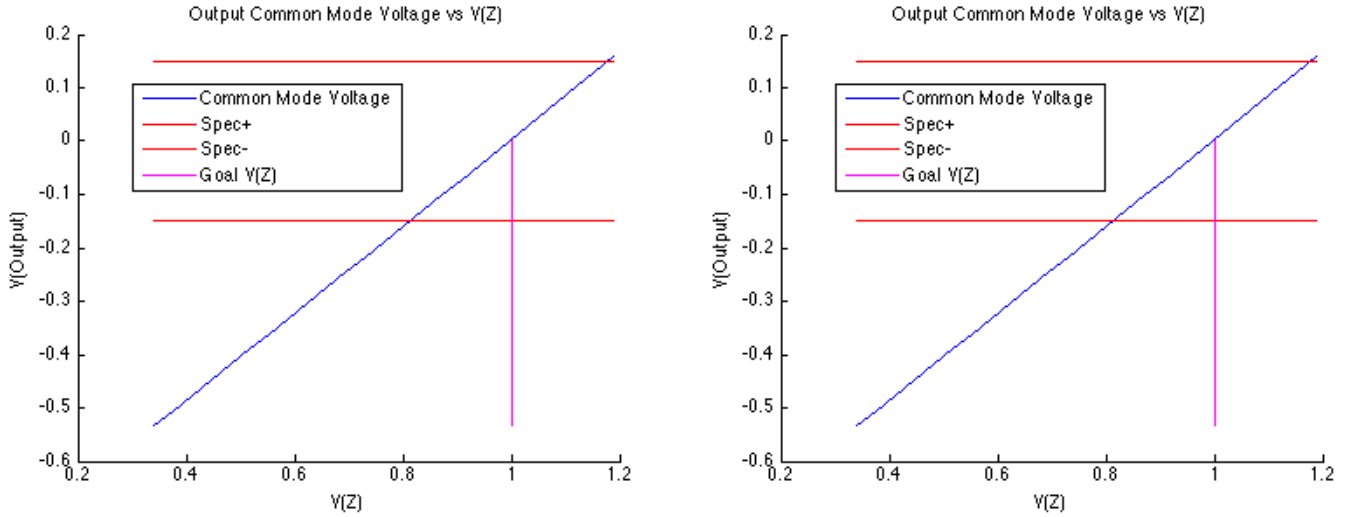

These graphs give rise to a process to choose exactly the value of those voltages based on the size of the transistors. Here, given the common mode output spec, choosing a size for MN10, and estimating the MN10 backgate gives the needed value of V_z . Given a size ratio for MN7 to MP8 gives the needed value of V_y , knowing V_z . Given the size ratio for MP4 to MN6 and knowing the value of V_y gives the necessary ratio of R3 to R4 to program the value of V_y .

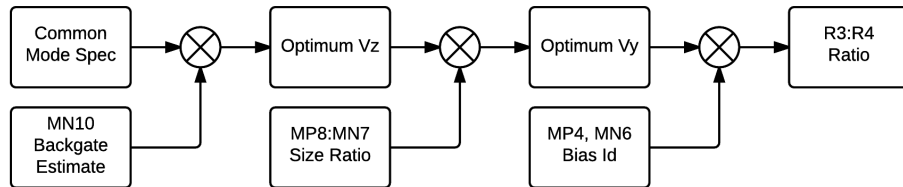

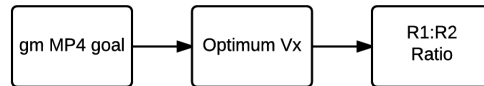Similarly for V_x , given a goal for MP4 gm (from our chosen distribution of stage gain) we can solve for the ratio of R1 to R2 to program the value of V_x . Since we have set the K value of MN1 and MP3 equal, the voltage at V_x is selected purely by the ratio of R1 and R2.




Once the math was developed to decouple the selection of stage gain to the DC biasing selection, the focus was on gain/speed. First we distributed the desired gain for each stage, then choose the v_{ov} level to drive the transistors based on the gm/Id plots, and then sized the transistors to minimize tau for adjacent stages.


The gain budget was based on the X stage having the most gain, since it's easy to get there, getting the balance of gain from the Y stage and then setting the Z stage to cancel out the gain loss of the output CD stage. Thus total gain simplifies to $X * Y = 30k$.

By making plots of the sum of tau for adjacent stages vs critical transistor sizing we were able to minimize total tau for the design, with the given gain budget.

2 Design Schematic

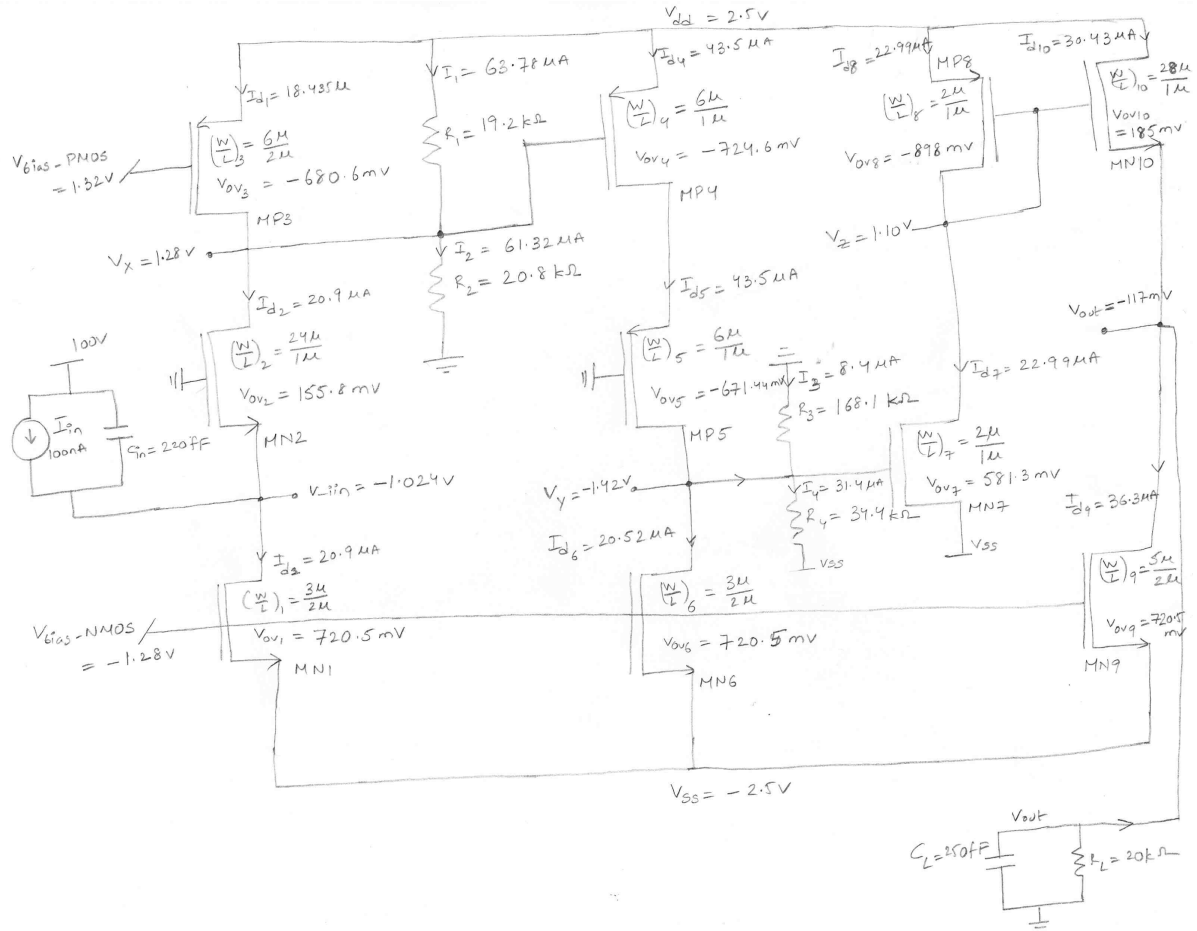

BIAS GENERATOR

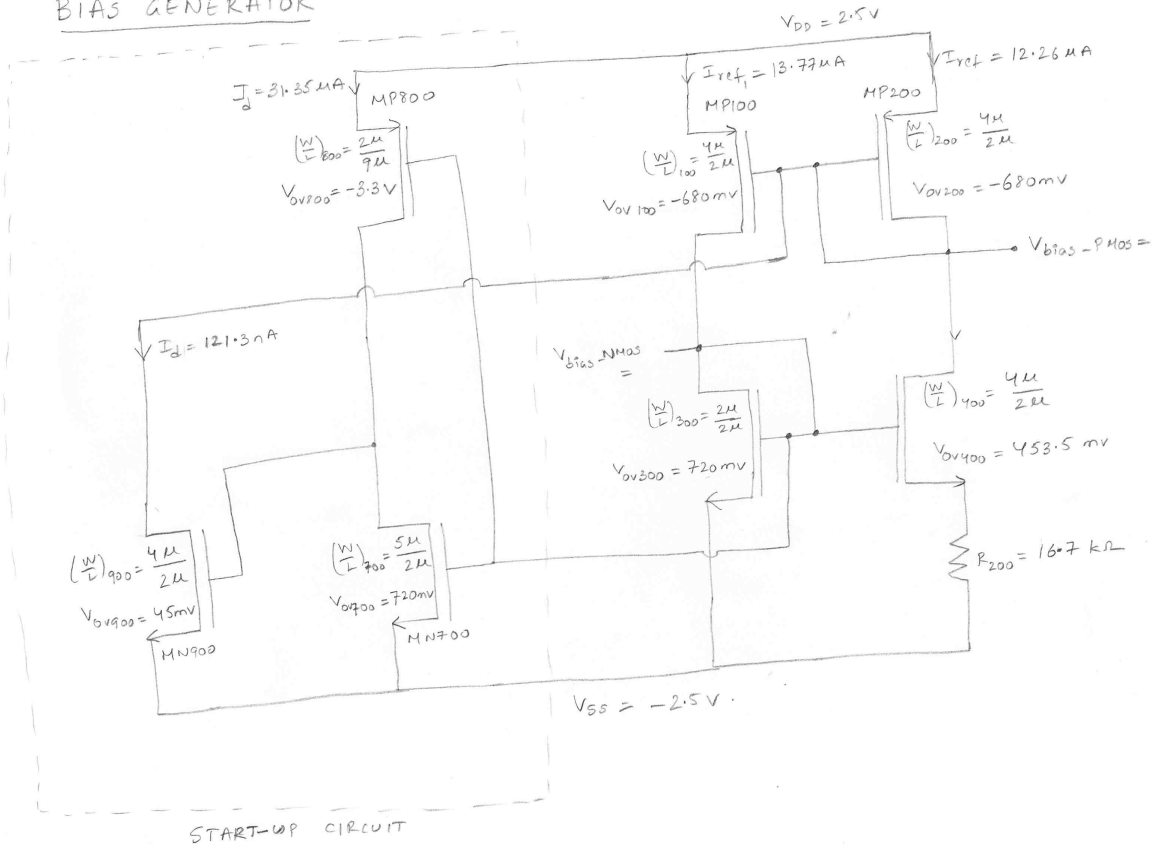

START-UP CIRCUIT

¹Drawings also attached to end of appendix in full size

3 Calculation of Key Design Parameters

Choice of L

- All devices used in current source have a minimum length of $2\mu\text{m}$.
- All other devices in the amplifier have minimum length of $1\mu\text{m}$. Minimum length is used as f_t is inversely proportional to L.
- All devices in bias generator circuit have length $\geq 2\mu\text{m}$.

Bias Generator circuit

- Constant gm reference based design is used as bias circuit to reduce mismatch errors.
- Transconductance of bias device (mn300) depends only on R2 and m (m is the ratio of MN300/MN400). Therefore gm can be set precisely.
- Start-up circuit is used to force the circuit to the desired operating point.

Approximations for hand calculations

For simpler hand calculations, following approximations are used.

1. $C_{db} = C_{sb} = 0.35C_{gs}$
2. $C_{gs} = (\frac{2}{3})WLCox + C_{ov}'W$
3. $C_{gd} = C_{ov}'W$
4. $g_{mb} = 0.2g_m$

Stage4

- As per the spec, common mode output voltage (v_{out}) has to be within -0.15v to 0.15v. Since the body is connected to vss, MN10 experiences back gate effect and the threshold voltage is given by:

$$\begin{aligned} V_t &= V_{t0} + \gamma(\sqrt{2\phi_f + V_{sb}} - \sqrt{2\phi_f}) \\ V_{t0} &= 0.5V, \gamma = 0.6, 2\phi_f = 0.8 \end{aligned} \quad (1)$$

- Stage 4 is a source follower which has a gain given by

$$A4 = \frac{g_{m_{10}}}{g_{m_{10}} + g_{mb_{10}} + (\frac{1}{R_L})} \quad (2)$$

- Gain of stage4 ($A4$) < 1 due to back gate effect and the output load.
- To achieve gain closer to 1 (0.6 - 0.7), it is important to size and bias MN10 such that $(g_{m_{10}} + g_{mb_{10}}) \gg (1/R_L)$.
- Transconductance of and drain current of MN_{10} is given by

$$g_{m_{10}} = \mu_n C_{ox} (\frac{W}{L}) v_{ov_{10}} \quad (3)$$

$$I_{d_{10}} = 0.5\mu_n C_{ox} (\frac{W_{10}}{L_{10}}) v_{ov_{10}}^2 (1 + \lambda(V_{dd} - V_{out})) \quad (4)$$

- MN_9 (bias device for source follower) is sized such that $Id_{10} + I_{RL} = Id_9$ and the common mode output voltage does not fall out of range. This device is chosen to be of smaller size to reduce loading on Vout node.

$$\tau_{OUTPUT} = (R_L || \frac{1}{1.2gm_{10}})(C_L + Csb_{10} + Cgd_9 + Cdb_9) \quad (5)$$

- Cgs_{10} is assumed to be very small due to boot-strapping.

Stage 3

- Loading at node Vy increases with the increase in gain of stage 3 due to the miller effect. Hence gain of stage3 is kept low and is fixed at $\sqrt{2}$ to compensate for the gain lost in stage 4. Gain of stage3 (CS amplifier with diode connected load):

$$|A3| = \frac{gm_7}{gm_8} = \frac{Vov_8}{Vov_7} = \frac{Vdd - Vz - abs(Vtp)}{Vy - Vss - Vtn} = \sqrt{2} \quad (6)$$

- Choice of Vz from above (stage4) determines Vy.
- Minimum device sizes ($W=2\mu m$, $L=1\mu m$) are used for both MN7 and MP8 to reduce loading on Vy and Vz.

$$Id_7 = Id_8 = 0.5\mu nCox(\frac{W_7}{L_7})vov_7^2(1 + \lambda(Vz - Vss)) \quad (7)$$

$$\tau_Z = (\frac{1}{gm_8})(Cgs_8 + Cdb_8 + Cgd_{10} + Cgd_7(1 + \frac{1}{|A3|}) + Cdb_7) \quad (8)$$

Stage 2


- Vy from stage Z above determines the required ratio of R3 and R4.

$$(\frac{R4}{R3}) = \frac{Vss}{Vy} - 1 \quad (9)$$

- Gain of stage Y (Cascode amplifier) is set to 3.

$$|A2| = gm_4(R3 || R4) \quad (10)$$

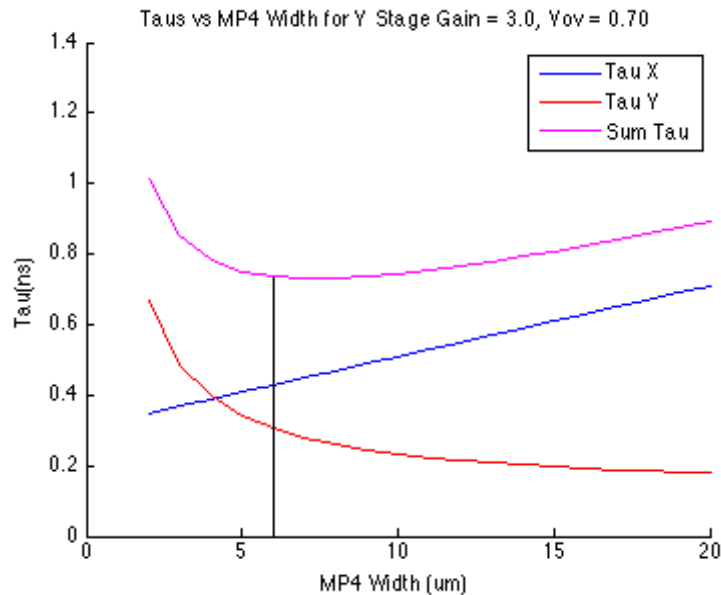- Vov_4 and W_4 are optimized to reduce τ_X .



- MN6 is sized such that current through MN6 is same as the current through MP4 and MP5.

$$Id4 = Id5 = Id6 = 0.5\mu pCox(\frac{W4}{L4})(Vdd - Vx - abs(Vtp))^2(1 + \lambda(Vdd - Vw)) \quad (11)$$

- Current through R3 and R4

$$I_{R3} + I_{R4} = Vss/(R3 + R4) \quad (12)$$

$$\tau_Y = (R3||R4)(Cgs7 + Cgd7(1 + |A3|) + Cgd6 + Cdb6 + Cgd5 + Cdb5) \quad (13)$$

Stage 1

- $Vov4$ from stage 2 sets V_X which in turn sets the ratio of R1 and R2.

$$Vov4 = Vdd - Vx - |Vtp| \quad (14)$$

$$(\frac{R1}{R2}) = \frac{Vdd}{Vx} - 1 \quad (15)$$


- Gain of stage 1 (Common gate amplifier) is set to 10000.

$$|A1| = (R1||R2) \quad (16)$$

- MN1 and MP3 are sized such that $Id1 = Id3$.
- MN2 is sized to reduce τ_{IIN} node. τ_{IIN} is inversely proportional to gm_2 .

$$\tau_{IIN} = (\frac{1}{gm2})(Cin + Cgd1 + Cdb1 + Cgs2 + Csb2) \quad (17)$$

$$\tau_X = (R1||R2)(Cgd2 + Cdb2 + Cgd3 + Cdb3 + Cgs4 + Cgd4) \quad (18)$$

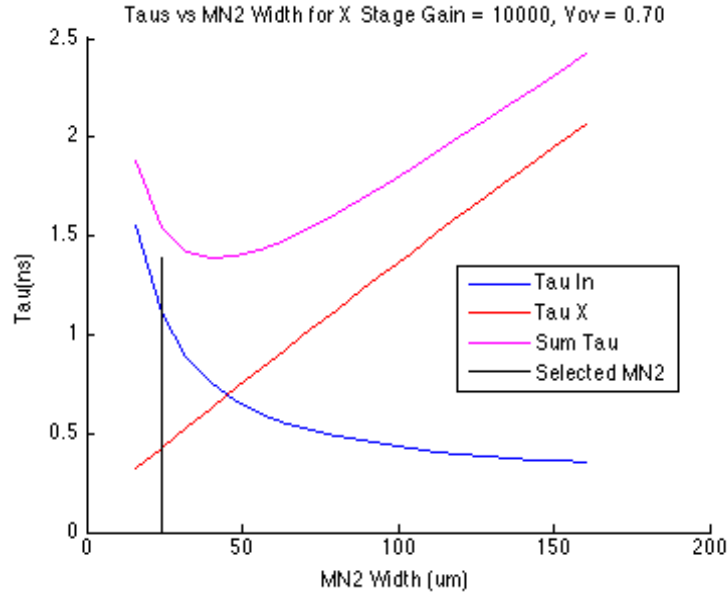

- Current through MN1, MN2 and MP3

$$Id_{1,2,3} = 0.5\mu pCox(\frac{W3}{L3})(Vdd - VbiasP - |Vtp|)^2(1 + \lambda(Vdd - Vx)) \quad (19)$$

- Current through R1 and R2

$$I_{R1} + I_{R2} = Vdd/(R1 + R2) \quad (20)$$

Vovn, Vovp

- Vovn and Vovp are chosen to achieve a reasonable balance between gain, Tau total and Power, and our choice was educated by the gm/Id technology plots.

Total Design Performance



$$|A_{TOTAL}| = A1 * A2 * A3 * A4 \quad (21)$$

$$\tau_{TOTAL} = \tau_{IN} + \tau_X + \tau_Y + \tau_Z + \tau_{OUTPUT} \quad (22)$$


$$Power = (V_{dd} - V_{ss})(I_{d1} + I_{d4} + I_{d7} + I_{d10}) + \left(\frac{V_{dd}^2}{R1 + R2}\right) + \left(\frac{V_{ss}^2}{R3 + R4}\right) \quad (23)$$

| Bias Generator | Hand calc | Spice | %Error | Reason for error |
|----------------|-----------------|-----------------|--------|---|
| V_{BiasN} | -1.300V | -1.279V | -1.6% | Startup circuit bias |
| V_{BiasP} | 1.300V | 1.319V | 1.5% | Startup circuit bias |
| | | | | |
| Stage1 | Hand calc | Spice | %Error | Reason for error |
| I_{d1} | 18.3 μ A | 20.9 μ A | 14.2% | Bias generator error |
| V_X | 1.300V | 1.275V | -1.9% | |
| A_X | 10k Ω | 9.86k Ω | -1.4% | Finite MN_1 and MP_3 output resistance |
| gm_2 | 210 μ S | 268 μ S | 27.6% | Bias generator error |
| τ_{IN} | 1.11ns | | | |
| τ_X | 420ps | | | |
| | | | | |
| Stage2 | Hand calc | Spice | %Error | Reason for error |
| I_{d4} | 36.75 μ A | 43.5 μ A | 18.4% | |
| V_W | 1.496V | 1.450V | -3.2% | |
| V_Y | -1.550V | -1.418V | -8.5% | Imbalance between MP_4 and MN_6 current |
| gm_4 | 105 μ S | 120 μ S | 14.3% | Error in V_Y |
| A_Y | -3.0 | -3.25 | 8.3% | Error estimating gm_4 |
| τ_Y | 306ps | | | |
| | | | | |
| Stage3 | Hand calc | Spice | %Error | Reason for error |
| I_{d7} | 10.25 μ A | 22.9 μ A | 123% | Error in V_Y plus finite output resistance |
| V_Z | 1.364 | 1.102V | -19.2% | Error in V_Y |
| gm_7 | 45 μ S | 79 μ S | 75.5% | Error in I_{d7} |
| gm_8 | 31.2 μ S | 51 μ S | 63.5% | Error in I_{d7} |
| A_Z | 1.414 | 1.440 | 1.8% | The benefit of ratiometric design |
| τ_Z | 1.92ns | | | Error in estimating gm_8 |
| | | | | |
| Stage4 | Hand calc | Spice | %Error | Reason for error |
| I_{d10} | 2.96 μ A | 30.43 μ A | 928% | MN_{10} 's large width is a big error amplifier |
| V_{OUT} | 0.299 | -0.117V | -139% | |
| V_{t10} | 0.999 | 1.034V | 3.5% | |
| gm_{10} | 91.1 μ S | 327 μ S | 258% | |
| gmb_{10} | 13.0 μ S | 55.1 μ S | 323% | |
| A_{OUT} | 0.71 | 0.75 | 5.6% | |
| τ_{OUT} | 1.63ns | | | Error in estimating gm_{10} |
| Total Power | 578 μ W | 1.065mW | 84% | Not accounting for bias gen |
| Total Gain | 30.04k Ω | 34.66k Ω | 15.5% | Error in estimating gm |

4 Simulated Bode Plots

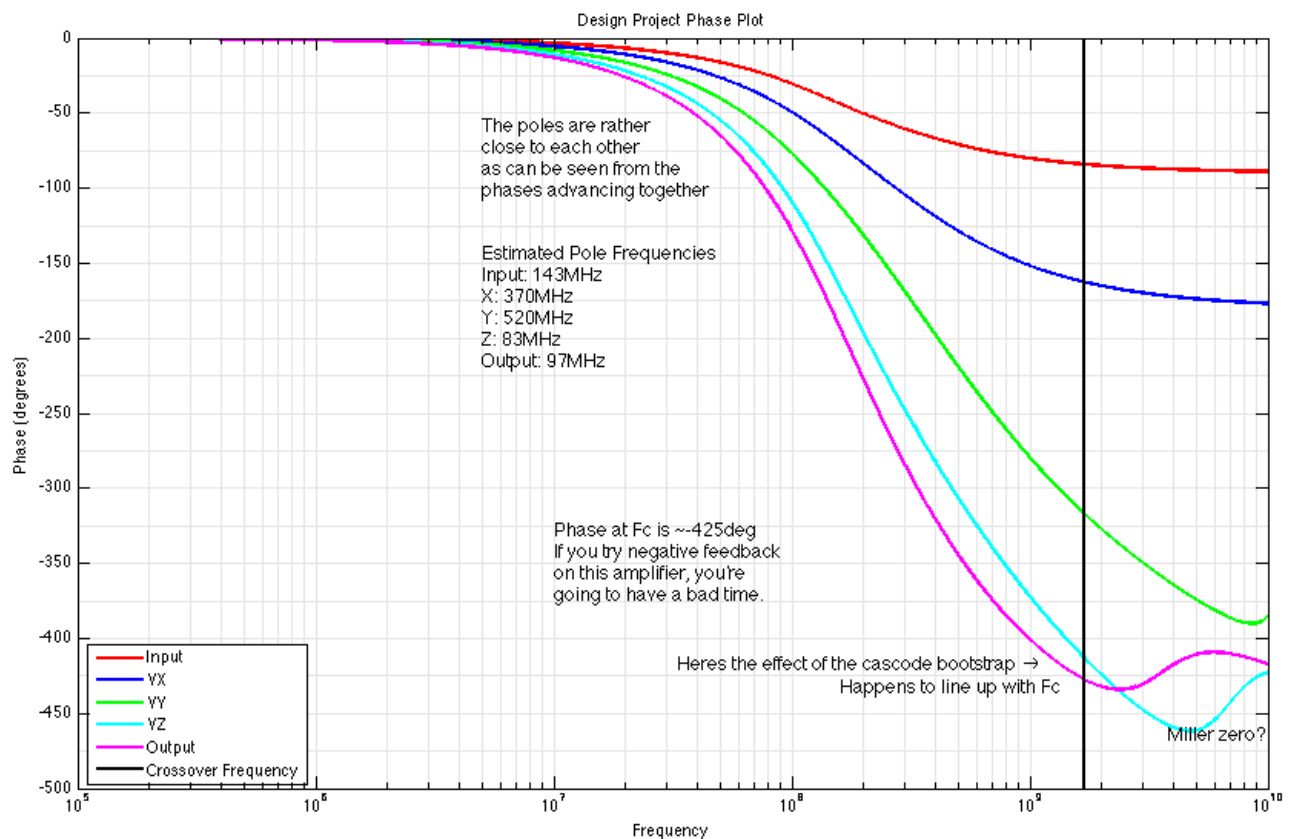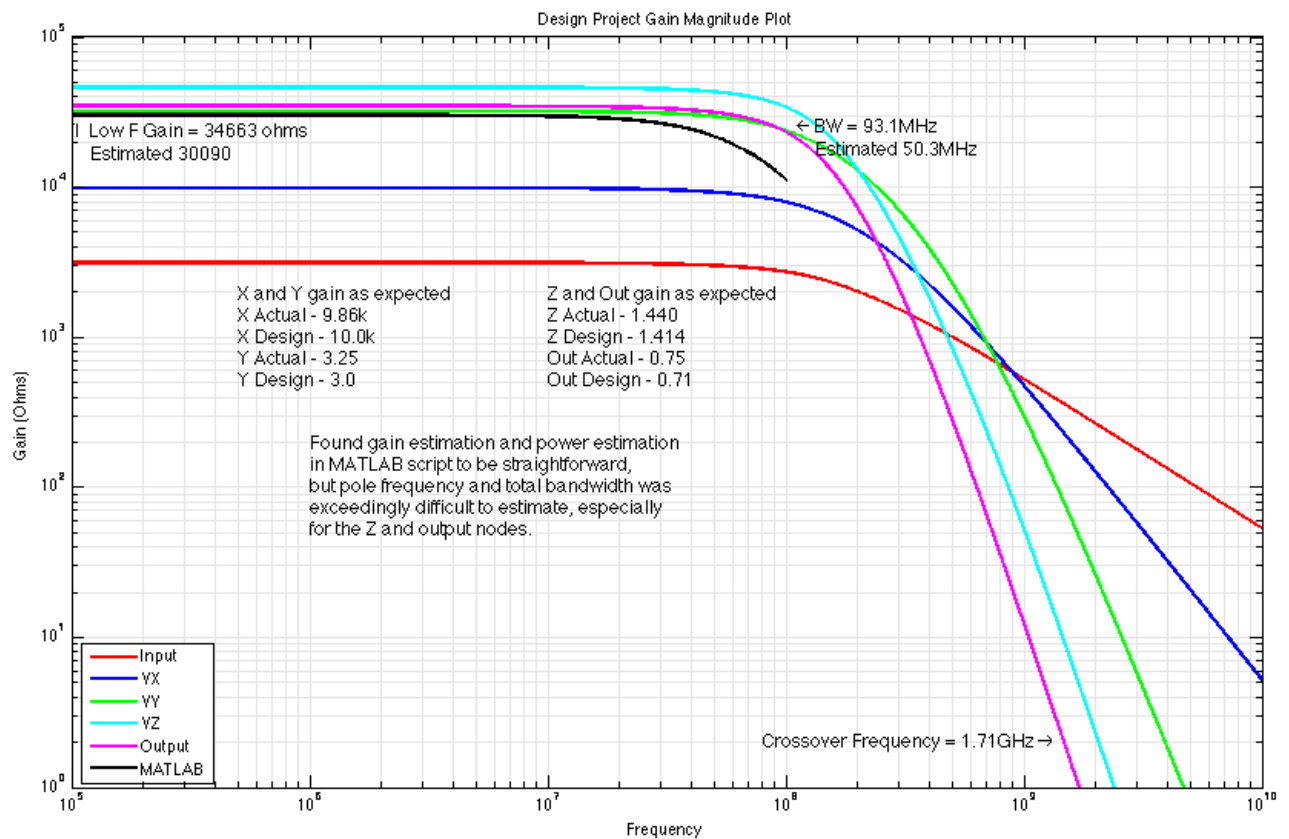

5 Simulated Transient Response

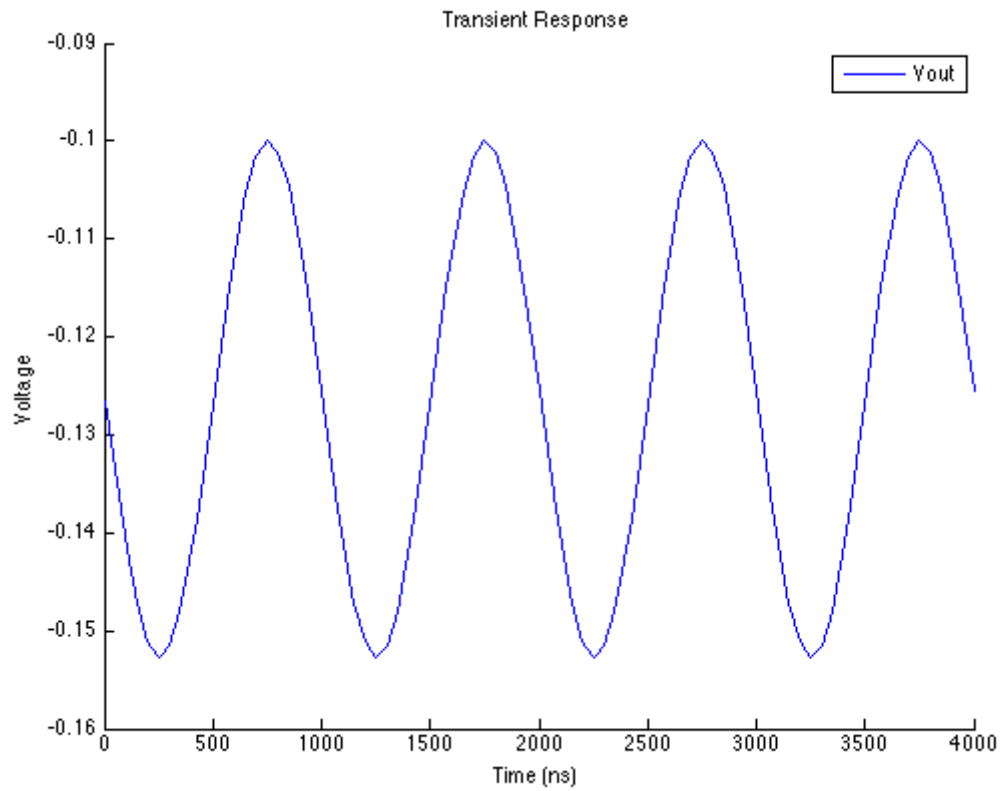

6 Comments and Conclusion

6.1 Notes about Design

- Resistors contribute to a large part of the overall gain. From manufacturability perspective, passive components are not friendly and also occupy more area on the chip. We feel that while the large value resistors helped us achieve a high gain and low power that they result in a possibly overly academic design that is not suitable for actual production.
- The output source follower stage is very sensitive to biasing due to back gate effect. Small variations on V_Z can drive the output to fall out of desired common mode voltage or drive MN_{10} into cutoff region and lose all the gain from previous stages.
- Any variations in supply voltage causes variation in V_{ov} of MN_7 directly (as the device is biased through R_3 & R_4) causing V_Z to vary and thereby impacting the biasing of MN_{10} and gain. This is a great node to lose any and all PSRR.
- Common source stage with diode connected load attributes to miller cap loading effect on cascade stage. This is limiting the gain of common source stage to smaller values.
- Since the output is single ended, it is susceptible to noise, a differential configuration will be better.

6.2 Notes on Project

- We found it very difficult to balance the many simultaneous requirements, and I felt that this was a very useful exercise that's directly applicable to industry, and not only to chip design. Many times I have found myself trying to explore design spaces that have myriad of opposing non-orthogonal requirements. I feel like I have learned interesting ways to approach these problems both mathematically and strategically.

7 Appendix I

7.1 SPICE Netlist

```
1 * Design Problem, ee114/214A-2015
2 * Team Member 1 Name: Usha Kankanala
3 * Team Member 2 Name: Samuel Lenius
4 * Please fill in the specification achieved by your circuit
5 * before you submit the netlist
6 *****
7 * sunetids of team members:
8 *   ukankana@stanford.edu: 06091239
9 *   lenius@stanford.edu: 06091240
10 * The specification that this script achieves are:
11 * Power      1.06mW      <= 2.00 mW      Meets Spec
12 * Gain       34.6k0hm    >= 30.0 k0hm    Meets Spec
13 * BandWidth  93.0MHz     >= 90.0 MHz     Meets Spec
14 * FOM        3043        >= 1350        Meets Spec
15 *****
16
17 * Including the model file
18 .include /usr/class/ee114/hspice/ee114_hspice.sp
19
20 * Defining Top level circuit parameters
21 .param p_Cin = 220f
22 .param p_CL  = 250f
23 .param p_RL  = 20k
24
25 * Defining the supply voltages
26 vdd      n_vdd  0      2.5
27 vss      n_vss  0      -2.5
28
29 *Defining the input current source
30 ** For ac simulation uncomment the following 2 lines**
31 Iin      n_iin  0      ac      100n
32 *Iin      n_iin  0      ac      1
33
34 ** For transient simulation uncomment the following 2 lines**
35 *Iin      n_iin  0      sin(0 0.5u 1e6)
36
37 * Defining Input capacitance
38 Cin      n_iin  0      'p_Cin'
39
40 * Defining the load
41 RL       n_vout  0      'p_RL'
42 CL       n_vout  0      'p_CL'
43
44 *** Your Trans-impedance Amplifier here ***
45 ***      d      g      s      b      n/pmos114      w      l
46
47 *** Vx/Iin = V(n_x) / Iin, use "n_x" as the node label for Vx ***
48 MN1      n_iin  n_bias_n  n_vss  n_vss  nmos114 w=3.0u l=2.0u
49
50 * Increasing the size of MN2 here is a power-free trick to improve the input
51 * pole performance.
52 MN2      n_x     0      n_iin  n_vss  nmos114 w=28.0u l=1.0u
53 MP3      n_x     n_bias_p  n_vdd  n_vdd  pmos114 w=6.0u l=2.0u
54
55 * The parallel combination of these resistors provide the first stage gain.
56 R1       n_vdd  n_x      19200
57 R2       n_x     0      20800
58
59 *** Vy/Vx = V(n_y) / V(n_x), use "n_y" as the node label for Vy ***
```

```

60 * MP4 both provides gain to the second stage and provides most of the node
61 * capacitance to the first stage, hence it's sizing is a delicate balance.
62 MP4      n_w      n_x      n_vdd n_vdd  pmos114 w=6.0u l=1.0u
63 MP5      n_y      0        n_w      n_vdd  pmos114 w=6.0u l=1.0u
64 MN6      n_y      n_bias_n  n_vss  n_vss  nmos114 w=3.0u l=2.0u
65 * We used asymmetry on MN6 in order to make Vy faster, and allow a higher Vov on
66 * MN6 however it made selecting the resistor values a lot tougher.
67
68 * These resistors provide the second stage gain, when combined with gm4.
69 * Asymmetry in MN6:MP4 sizing leads to a bit of a wonky ratio as they need to
70 * account for the imbalanced current.
71 R3       n_y      0        168100
72 R4       n_y      n_vss    34400
73
74 *** Vz/Vy = V(n_z) / V(n_y), use "n_z" as the node label for Vz ***
75 * The size of these transistors sets up the gain of the third stage. Here it's
76 * approximately sqrt(2)
77 MN7      n_z      n_y      n_vss  n_vss  nmos114 w=2.0u l=1.0u
78 MP8      n_z      n_z      n_vdd  n_vdd  pmos114 w=2.0u l=1.0u
79
80 *** Vout/Vz = V(n_vout) / V(n_z), use "n_vout" as the node label for Vout ***
81 * MN10 is very tricky to bias right. You need to account for it's large Vt due
82 * to backgate and you tend to have a lot of error stacked up by the time that Vz
83 * is biased. Hence it required a small amount of monkeying to get it just right
84 * after we hand calculated the values.
85 MN9      n_vout  n_bias_n  n_vss  n_vss  nmos114 w=5.0u l=2.0u
86 MN10     n_vdd   n_z       n_vout n_vss  nmos114 w=28.0u l=1.0u
87
88 *** Your Bias Circuitry goes here ***
89
90 * This design is a self-biasing delta-Vgs / constant gm reference with startup
91 * circuit. The design was taken from lecture notes 14.
92
93 * These transistors provide the PMOS bias
94 MP100    n_bias_n n_bias_p n_vdd n_vdd  pmos114 w=4u  l=2u
95 MP200    n_bias_p n_bias_p n_vdd n_vdd  pmos114 w=4u  l=2u
96
97 * These transistors provide the NMOS bias and are the source of the delta
98 * Vgs reference. The ratio between the widths of these transistors defines m.
99 MN300    n_bias_n n_bias_n n_vss n_vss  nmos114 w=2u  l=2u
100 MN400    n_bias_p n_bias_n n_biasr2 n_vss nmos114 w=4u l=2u
101
102 * This resistor is the denominator of the reference vov equation.
103 R200     n_biasr2 n_vss    16.7k
104
105 * These transistors are the startup circuit that enforces that it stay at
106 * the upper stable point, as the system is bistable.
107 MP800    n_biasn9 n_bias_n n_vdd n_vdd  pmos114 w=2u  l=9u
108 MN700    n_biasn9 n_bias_n n_vss n_vss  nmos114 w=5u  l=2u
109 MN900    n_bias_p n_biasn9 n_vss n_vss  nmos114 w=4u  l=2u
110
111 *** defining the analysis ***
112 .op
113 .option post brief nomod
114
115 ** For ac simulation uncomment the following line**
116 .ac dec 1k 100 1g
117
118 .measure ac gainmax_vout max vdb(n_vout)
119 .measure ac f3db_vout when vdb(n_vout)='gainmax_vout-3'
120
121 .measure ac gainmax_vx max vdb(n_x)
122 .measure ac f3db_vx when vdb(n_x)='gainmax_vx-3'
123

```

```

124 .measure ac gainmax_vy max vdb(n_y)
125 .measure ac f3db_vy when vdb(n_y)='gainmax_vy-3'
126
127 .measure ac gainmax_vz max vdb(n_z)
128 .measure ac f3db_vz when vdb(n_z)='gainmax_vz-3'
129
130 ** For transient simulation uncomment the following line **
131 *.tran 0.01u 4u
132
133 .end

```

7.2 SPICE .op Output

```

1 ***** HSPICE -- I-2013.12-SP2 64-BIT (May 27 2014) RHEL64 *****
2 Copyright (C) 2014 Synopsys, Inc. All Rights Reserved.
3 Unpublished-rights reserved under US copyright laws.
4 This program is protected by law and is subject to the
5 terms and conditions of the license agreement from Synopsys.
6 Use of this program is your acceptance to be bound by the
7 license agreement. HSPICE is the trademark of Synopsys, Inc.
8 Input File: Final_Samuel_Lenius_Usha_Kankanala_1p0_34p6_93p0_3043.sp
9 Command line options: Final_Samuel_Lenius_Usha_Kankanala_1p0_34p6_93p0_3043.sp
10 lic:
11 lic: FLEXlm: v10.9.8
12 lic: USER: lenius HOSTNAME: corn27.stanford.edu
13 lic: HOSTID: 001b213a6bad PID: 9885
14 lic: Using FLEXlm license file:
15 lic: 27000@cadlic0
16 lic: Checkout 1 hspice
17 lic: License/Maintenance for hspice will expire on 09-jan-2016/2015.06
18 lic: 2(in_use)/200(total) FLOATING license(s) on SERVER 27000@cadlic0
19 lic:
20
21
22 *****
23 ***** option summary
24 *****
25 runlvl = 3 bypass = 2
26 **info** dc convergence successful at Newton-Raphson method
27 ***** HSPICE -- I-2013.12-SP2 64-BIT (May 27 2014) RHEL64 *****
28 *****
29 * design problem, ee114/214a-2015
30
31 ***** operating point information tnom= 25.000 temp= 25.000 *****
32 ***** operating point status is all simulation time is 0.
33 node =voltage node =voltage node =voltage
34
35 +0:n_bias_n= -1.2795 0:n_bias_p= 1.3194 0:n_biasn9= -1.9549
36 +0:n_biasr2= -2.2972 0:n_iin = -1.0243 0:n_vdd = 2.5000
37 +0:n_vout = -117.4867m 0:n_vss = -2.5000 0:n_w = 1.4507
38 +0:n_x = 1.2754 0:n_y = -1.4186 0:n_z = 1.1019
39
40
41 **** voltage sources
42
43 subckt
44 element 0:vdd 0:vss
45 volts 2.5000 -2.5000
46 current -236.5422u 189.5402u
47 power 591.3555u 473.8505u
48
49 total voltage source power dissipation= 1.0652m watts
50
51

```

```

52
53 **** current sources
54
55 subckt
56 element 0:iin
57 volts -1.0243
58 current 0.
59 power 0.
60
61
62 total current source power dissipation= 0. watts
63
64 **** resistors
65
66 subckt
67 element 0:r1 0:r1 0:r2 0:r3 0:r4 0:r200
68 r value 20.0000k 19.2000k 20.8000k 168.1000k 34.4000k 16.7000k
69 v drop -117.4867m 1.2246 1.2754 -1.4186 1.0814 202.7945m
70 current -5.8743u 63.7831u 61.3156u -8.4393u 31.4349u 12.1434u
71 power 690.1559n 78.1111u 78.1997u 11.9723u 33.9924u 2.4626u
72
73
74
75 **** mosfets
76
77
78 subckt
79 element 0:mn1 0:mn2 0:mp3 0:mp4 0:mp5 0:mn6
80 model 0:nmos114. 0:nmos114. 0:pmos114. 0:pmos114. 0:pmos114. 0:nmos114.
81 region Saturati Saturati Saturati Saturati Saturati Saturati
82 id 20.9028u 20.9028u -18.4353u -43.5146u -43.5146u 20.5190u
83 ibs 0. -14.7571f 0. 0. 10.4928f 0.
84 ibd -14.7571f -37.7536f 12.2464f 10.4928f 39.1864f -10.8136f
85 vgs 1.2205 1.0243 -1.1806 -1.2246 -1.4507 1.2205
86 vds 1.4757 2.2997 -1.2246 -1.0493 -2.8694 1.0814
87 vbs 0. -1.4757 0. 0. 1.0493 0.
88 vth 500.0000m 868.4718m -500.0000m -500.0000m -779.2740m 500.0000m
89 vdsat 720.4904m 155.8143m -680.6195m -724.6359m -671.4420m 720.4904m
90 vod 720.4904m 155.8143m -680.6195m -724.6359m -671.4420m 720.4904m
91 beta 80.5339u 1.7220m 79.5924u 165.7393u 193.0403u 79.0551u
92 gam eff 600.0000m 600.0000m 600.0000m 600.0000m 600.0000m 600.0000m
93 gm 58.0239u 268.3046u 54.1721u 120.1006u 129.6154u 56.9584u
94 gds 973.3246n 1.6995u 868.5804n 3.9382u 3.3813u 973.3246n
95 gmb 19.4618u 53.3569u 18.1699u 40.2830u 28.5941u 19.1044u
96 cdtot 5.3930f 27.9761f 9.8099f 10.0272f 7.8875f 5.6372f
97 cgtot 12.3208f 72.3462f 24.6430f 15.3124f 15.3250f 12.3136f
98 cstot 16.1000f 74.6671f 31.0001f 21.8000f 19.2080f 16.1000f
99 cbtot 9.3595f 32.7274f 16.5627f 16.7010f 11.9148f 9.6109f
100 cgs 10.7000f 56.9335f 21.4001f 12.2000f 12.2000f 10.7000f
101 cgd 1.5272f 14.1975f 3.0451f 3.0193f 3.0528f 1.5199f
102
103
104
105 subckt
106 element 0:mn7 0:mp8 0:mn9 0:mn10 0:mp100 0:mp200
107 model 0:nmos114. 0:pmos114. 0:nmos114. 0:nmos114. 0:pmos114. 0:pmos114.
108 region Saturati Saturati Saturati Saturati Saturati Saturati
109 id 22.9857u -22.9857u 36.3091u 30.4348u -13.7696u -12.2647u
110 ibs 0. 0. 0. -23.8251f 0. 0.
111 ibd -36.0186f 13.9814f -23.8251f -50.0000f 37.7951f 11.8062f
112 vgs 1.0814 -1.3981 1.2205 1.2194 -1.1806 -1.1806
113 vds 3.6019 -1.3981 2.3825 2.6175 -3.7795 -1.1806
114 vbs 0. 0. 0. -2.3825 0. 0.
115 vth 500.0000m -500.0000m 500.0000m 1.0337 -500.0000m -500.0000m

```

```

116 vdsat 581.3598m -898.1364m 720.4904m 185.6306m -680.6195m -680.6195m
117 vod 581.3598m -898.1364m 720.4904m 185.6306m -680.6195m -680.6195m
118 beta 136.0186u 56.9907u 139.8907u 1.7664m 59.4488u 52.9515u
119 gam_eff 600.0000m 600.0000m 600.0000m 600.0000m 600.0000m 600.0000m
120 gm 79.0758u 51.1854u 100.7899u 327.9067u 40.4620u 36.0399u
121 gds 1.6899u 2.0166u 1.6222u 2.4121u 579.0536n 579.0536n
122 gmb 26.5228u 17.1681u 33.8060u 55.1425u 13.5714u 12.0881u
123 cdtot 3.6813f 4.2306f 7.0089f 26.8604f 5.7669f 7.1139f
124 cgtot 5.1272f 5.1004f 20.5625f 72.0600f 16.4914f 16.4276f
125 cstot 8.6667f 8.6667f 24.8334f 72.6537f 21.3667f 21.3667f
126 cbtot 7.2976f 7.8472f 11.5918f 29.2575f 10.9061f 12.3169f
127 cgs 4.0667f 4.0667f 17.8334f 56.9335f 14.2667f 14.2667f
128 cgd 1.0221f 1.0086f 2.5731f 14.2248f 2.0927f 2.0290f
129
130
131
132 subckt
133 element 0:mn300 0:mn400 0:mp800 0:mn700 0:mn900
134 model 0:nmos114. 0:nmos114. 0:pmos114. 0:nmos114. 0:nmos114.
135 region Saturati Saturati Saturati Linear Saturati
136 id 13.7696u 12.1434u -31.3543u 31.3543u 121.3242n
137 ibs 0. -2.0279f 0. 0. 0.
138 ibd -12.2049f -38.1938f 44.5486f -5.4514f -38.1938f
139 vgs 1.2205 1.0177 -3.7795 1.2205 545.1376m
140 vds 1.2205 3.6166 -4.4549 545.1376m 3.8194
141 vbs 0. -202.7945m 0. 0. 0.
142 vth 500.0000m 564.1814m -500.0000m 500.0000m 500.0000m
143 vdsat 720.4904m 453.5145m -3.2795 545.1376m 45.1376m
144 vod 720.4904m 453.5145m -3.2795 720.4904m 45.1376m
145 beta 53.0512u 118.0829u 5.8305u 128.4071u 119.0969u
146 gam_eff 600.0000m 600.0000m 600.0000m 600.0000m 600.0000m
147 gm 38.2229u 53.5523u 19.1213u 69.9995u 5.3757u
148 gds 648.8830n 514.1885n 331.9501n 24.0427u 5.0935n
149 gmb 12.8204u 16.0433u 6.4135u 23.4786u 1.8031u
150 cdtot 4.4573f 5.5601f 3.5781f 13.8464f 5.5651f
151 cgtot 8.2107f 16.5346f 29.9091f 25.3172f 17.7794f
152 cstot 11.7334f 20.0468f 33.2001f 24.2459f 20.4667f
153 cbtot 8.1048f 9.4306f 6.9952f 13.0872f 11.0903f
154 cgs 7.1334f 14.2667f 28.6001f 17.2459f 14.2667f
155 cgd 1.0150f 2.0887f 1.2459f 7.9152f 2.0937f
156
157
158
159 *****
160 * design problem, ee114/214a-2015
161
162 ***** ac analysis tnom= 25.000 temp= 25.000 *****
163 gainmax_vout= -49.2028 at= 5.3333k
164 from= 100.0000 to= 1.0000g
165 f3db_vout= 92.9703x
166 gainmax_vx= -60.1155 at= 36.1410k
167 from= 100.0000 to= 1.0000g
168 f3db_vx= 131.9439x
169 gainmax_vy= -49.8772 at= 21.4289k
170 from= 100.0000 to= 1.0000g
171 f3db_vy= 108.3150x
172 gainmax_vz= -46.7065 at= 21.3304k
173 from= 100.0000 to= 1.0000g
174 f3db_vz= 105.6056x
175
176 ***** job concluded
177 ***** HSPICE -- I-2013.12-SP2 64-BIT (May 27 2014) RHEL64 *****
178 *****
179 * design problem, ee114/214a-2015


```

```

180
181 ***** job statistics summary tnom= 25.000 temp= 25.000 *****
182
183
184 ***** Machine Information *****
185 CPU:
186 model name      : Quad-Core AMD Opteron(tm) Processor 2384
187 cpu MHz        : 800.000
188
189 OS:
190 Linux version 3.13.0-53-generic (buildd@phianna) (gcc version 4.8.2 (Ubuntu
    4.8.2-19ubuntu1) ) #89-Ubuntu SMP Wed May 20 10:34:39 UTC 2015
191
192
193 ***** HSPICE Threads Information *****
194
195 Command Line Threads Count :      1
196 Available CPU Count        :      8
197 Actual Threads Count       :      1
198
199
200 ***** Circuit Statistics *****
201 # nodes      =      13 # elements  =      28
202 # resistors  =      6 # capacitors =      2 # inductors  =      0
203 # mutual_inds =      0 # vccs      =      0 # vcvs      =      0
204 # cccs       =      0 # ccvs      =      0 # volt_srcs =      2
205 # curr_srcs  =      1 # diodes   =      0 # bjts      =      0
206 # jfets      =      0 # mosfets =      17 # U elements =      0
207 # T elements =      0 # W elements =      0 # B elements =      0
208 # S elements =      0 # P elements =      0 # va device  =      0
209 # vector_srcs =      0 # N elements =      0
210
211
212 ***** Runtime Statistics (seconds) *****
213
214 analysis      time      # points  tot. iter  conv.iter
215 op point      0.00      1         10
216 ac analysis    0.08      7001     7001
217 readin        0.01
218 errchk        0.00
219 setup         0.00
220 output        0.00
221
222
223          peak memory used      176.94 megabytes
224          total cpu time        0.09 seconds
225          total elapsed time    1.19 seconds
226          job started at      06:46:11 12/04/2015
227          job ended   at      06:46:13 12/04/2015
228
229
230 lic: Release hspice token(s)
231 lic: total license checkout elapse time:      1.01(s)

```


7.3 Amplifier - Enlarged

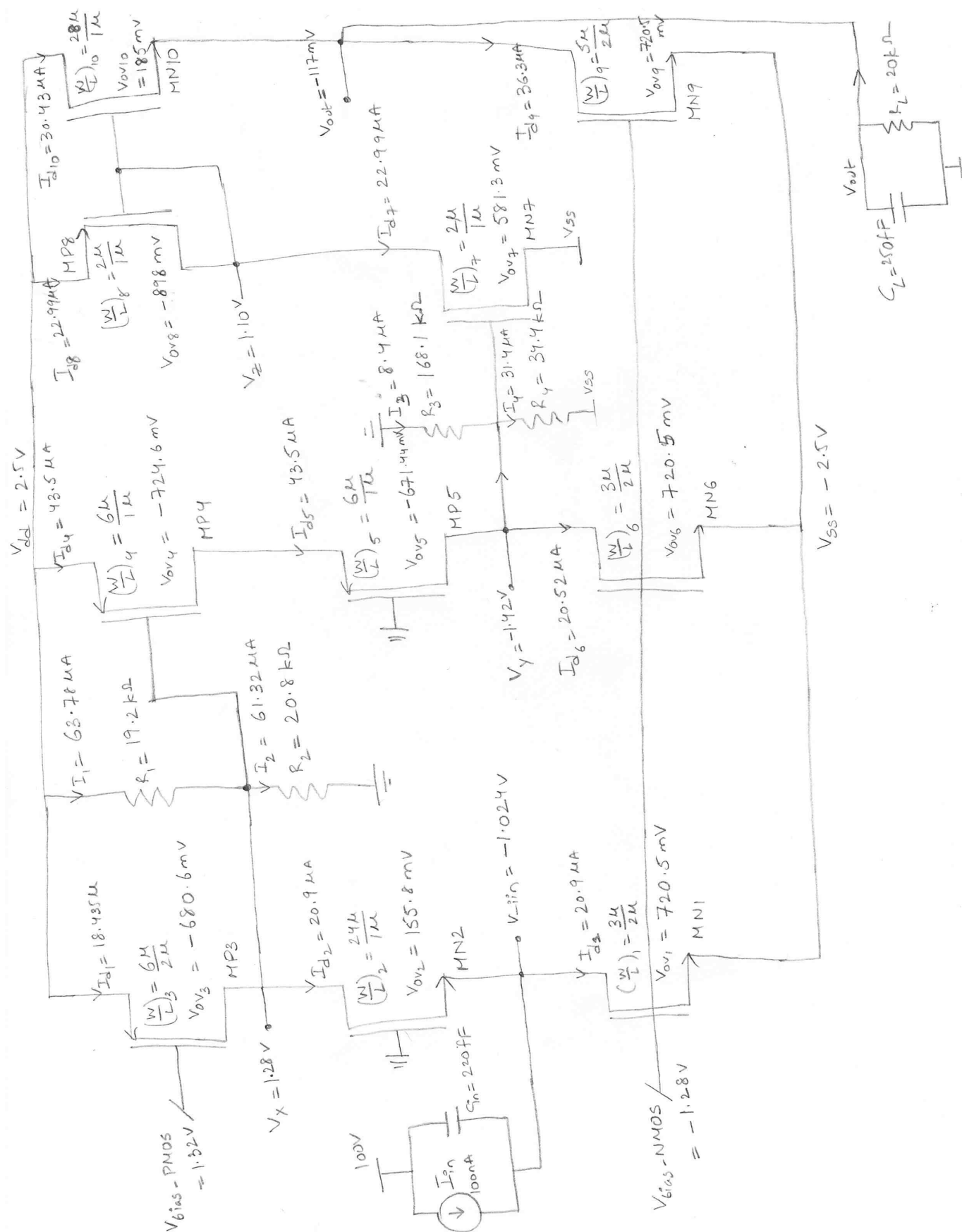

7.4 Bias Circuit - Enlarged

