

# 2015 EE214A Design Project

Kankanala, Usha  
ukankana@stanford.edu  
SUID:06091239

Lenius, Samuel  
lenius@stanford.com  
SUID:06091240


December 4, 2015

<b>Specifications</b>	Given Spec	Achieved Spec
Gain	30k $\Omega$	34.7k $\Omega$
Bandwidth	90MHz	93MHz
Power	2.0mW	1.0mW
FOM	1350	3043


<b>Area Breakdown</b>	% Core Area	Area ( $\mu\text{m}$ )
Core Area	100%	112 $\mu\text{m}^2$
VNMOS-bias	19.6%	22 $\mu\text{m}^2$
VP MOS-bias	10.7%	12 $\mu\text{m}^2$
Bias Generator	73.1%	82 $\mu\text{m}^2$
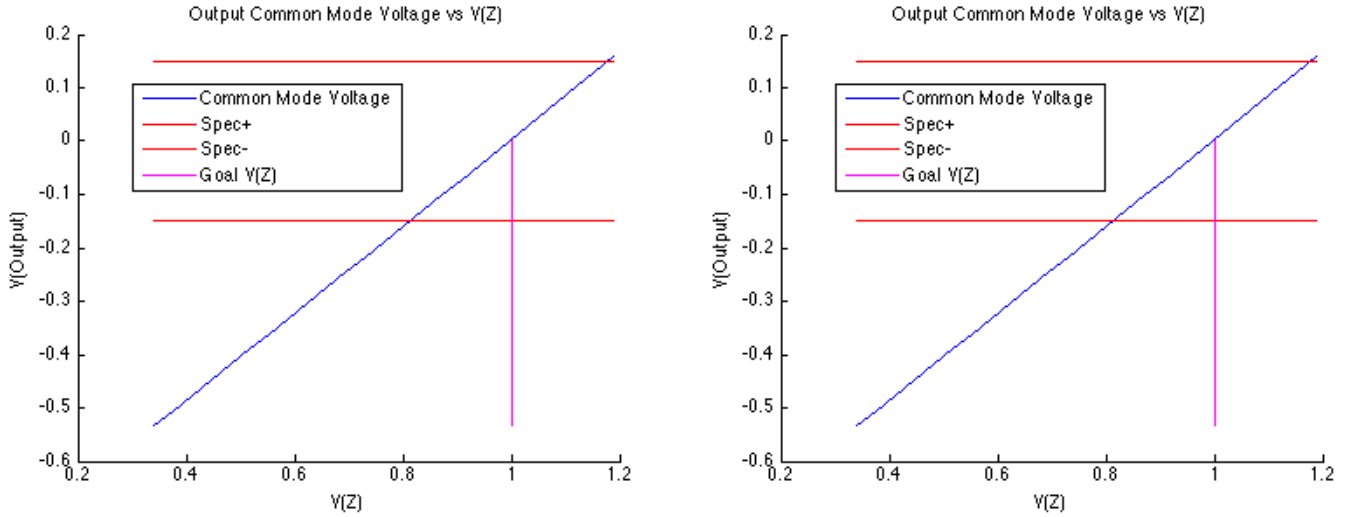
# 1 Design Outline


Our approach to this design was to first develop sizing ratios of the transistors and their DC relationships to  $V_x$ ,  $V_y$ ,  $V_z$  and  $V_o$ . We developed the equations necessary to ‘program’ those voltages and to develop what their reasonable ranges are. Here are some graphs that show the relationships between the output common mode voltage and  $V_z$ , and then  $V_z$  to  $V_y$  given our sizing decisions. We developed a MATLAB program to quickly estimate critical parameters for a given design, to allow easy investigation of parametric variation.



These graphs give rise to a process to choose exactly the value of those voltages based on the size of the transistors. Here, given the common mode output spec, choosing a size for MN10, and estimating the MN10 backgate gives the needed value of  $V_z$ . Given a size ratio for MN7 to MP8 gives the needed value of  $V_y$ , knowing  $V_z$ . Given the size ratio for MP4 to MN6 and knowing the value of  $V_y$  gives the necessary ratio of R3 to R4 to program the value of  $V_y$ .

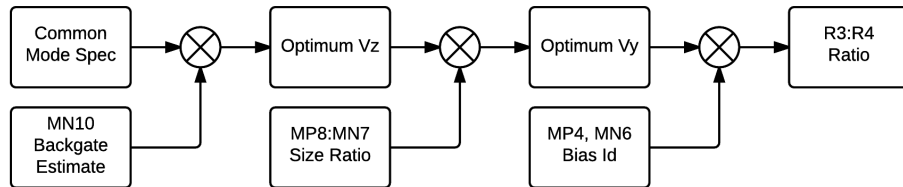

 Similarly for  $V_x$ , given a goal for MP4 gm (from our chosen distribution of stage gain) we can solve for the ratio of R1 to R2 to program the value of  $V_x$ . Since we have set the K value of MN1 and MP3 equal, the voltage at  $V_x$  is selected purely by the ratio of R1 and R2.




Once the math was developed to decouple the selection of stage gain to the DC biasing selection, the focus was on gain/speed. First we distributed the desired gain for each stage, then choose the  $v_{ov}$  level to drive the transistors based on the gm/Id plots, and then sized the transistors to minimize tau for adjacent stages.


The gain budget was based on the X stage having the most gain, since it's easy to get there, getting the balance of gain from the Y stage and then setting the Z stage to cancel out the gain loss of the output CD stage. Thus total gain simplifies to  $X * Y = 30k$ .

By making plots of the sum of tau for adjacent stages vs critical transistor sizing we were able to minimize total tau for the design, with the given gain budget.

## 2 Design Schematic

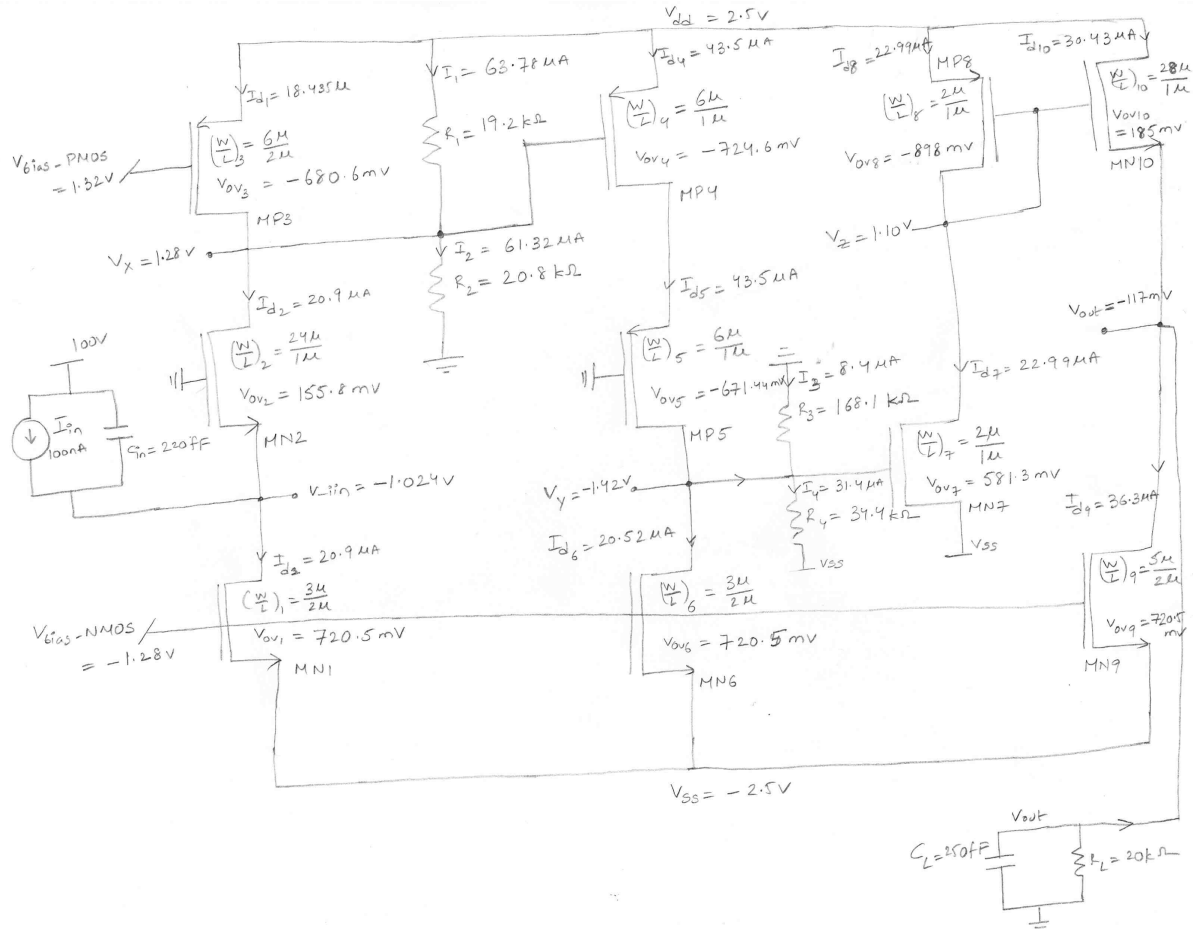

### BIAS GENERATOR

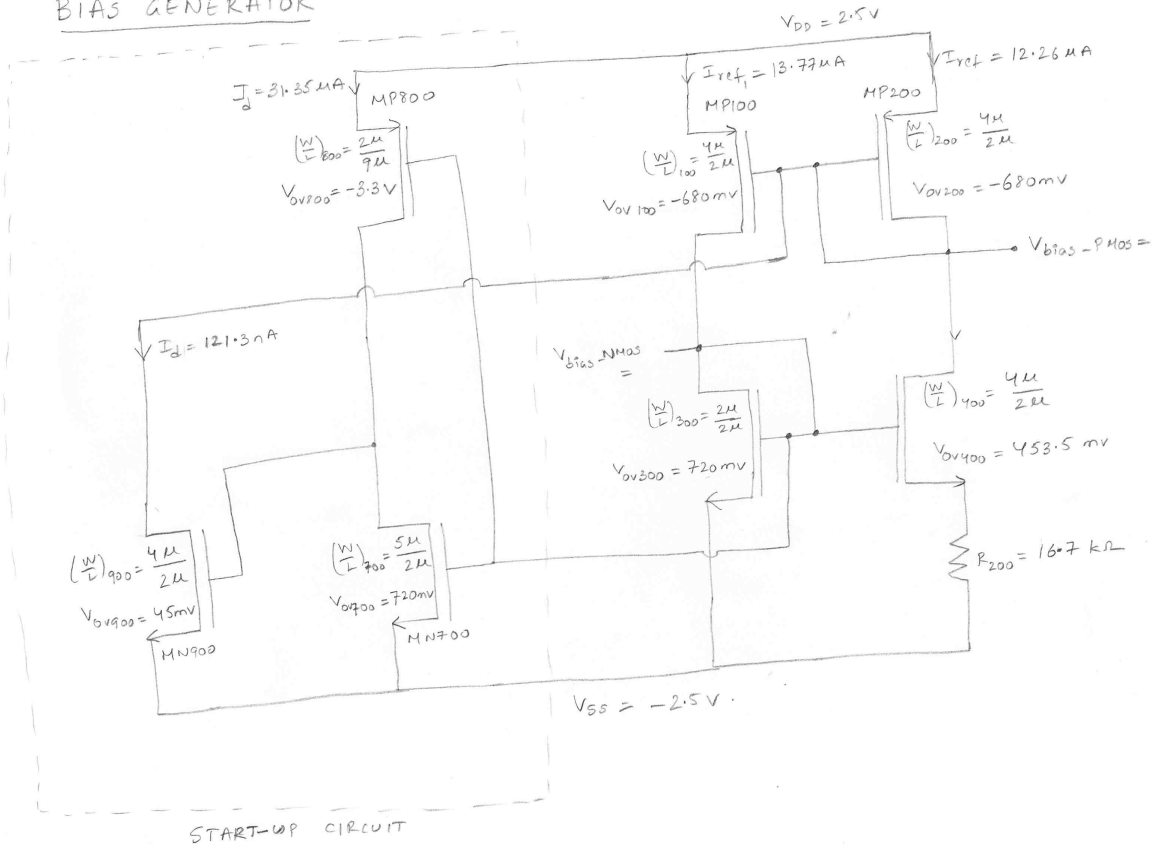

START-UP CIRCUIT

<sup>1</sup>Drawings also attached to end of appendix in full size

### 3 Calculation of Key Design Parameters

#### Choice of L

- All devices used in current source have a minimum length of  $2\mu\text{m}$ .
- All other devices in the amplifier have minimum length of  $1\mu\text{m}$ . Minimum length is used as  $f_t$  is inversely proportional to L.
- All devices in bias generator circuit have length  $\geq 2\mu\text{m}$ .

#### Bias Generator circuit

- Constant gm reference based design is used as bias circuit to reduce mismatch errors.
- Transconductance of bias device (mn300) depends only on R2 and m ( m is the ratio of MN300/MN400). Therefore gm can be set precisely.
- Start-up circuit is used to force the circuit to the desired operating point.

#### Approximations for hand calculations

For simpler hand calculations, following approximations are used.

1.  $C_{db} = C_{sb} = 0.35C_{gs}$
2.  $C_{gs} = (\frac{2}{3})WLCox + Cov'W$
3.  $C_{gd} = Cov'W$
4.  $g_{mb} = 0.2gm$

#### Stage4

- As per the spec, common mode output voltage (vout) has to be within -0.15v to 0.15v. Since the body is connected to vss, MN10 experiences back gate effect and the threshold voltage is given by:

$$\begin{aligned} Vt &= Vt_0 + \gamma(\sqrt{2\phi f + V_{sb}} - \sqrt{2\phi f}) \\ Vt_0 &= 0.5V, \gamma = 0.6, 2\phi f = 0.8 \end{aligned} \quad (1)$$

- Stage 4 is a source follower which has a gain given by

$$A4 = \frac{gm_{10}}{gm_{10} + g_{mb_{10}} + (\frac{1}{R_L})} \quad (2)$$

- Gain of stage4 ( $A4$ )  $< 1$  due to back gate effect and the output load.
- To achieve gain closer to 1 (0.6 - 0.7), it is important to size and bias MN10 such that  $(gm_{10} + g_{mb_{10}}) \gg (1/R_L)$ .
- Transconductance of and drain current of  $MN_{10}$  is given by

$$gm_{10} = \mu n Cox (\frac{W}{L}) vov_{10} \quad (3)$$

$$Id_{10} = 0.5\mu n Cox (\frac{W_{10}}{L_{10}}) vov_{10}^2 (1 + \lambda(V_{dd} - V_{out})) \quad (4)$$

- $MN_9$  (bias device for source follower) is sized such that  $Id_{10} + I_{RL} = Id_9$  and the common mode output voltage does not fall out of range. This device is chosen to be of smaller size to reduce loading on Vout node.

$$\tau_{OUTPUT} = (R_L || \frac{1}{1.2gm_{10}})(C_L + Csb_{10} + Cgd_9 + Cdb_9) \quad (5)$$

- $Cgs_{10}$  is assumed to be very small due to boot-strapping.

### Stage 3

- Loading at node Vy increases with the increase in gain of stage 3 due to the miller effect. Hence gain of stage3 is kept low and is fixed at  $\sqrt{2}$  to compensate for the gain lost in stage 4. Gain of stage3 (CS amplifier with diode connected load):

$$|A3| = \frac{gm_7}{gm_8} = \frac{Vov_8}{Vov_7} = \frac{Vdd - Vz - abs(Vtp)}{Vy - Vss - Vtn} = \sqrt{2} \quad (6)$$

- Choice of Vz from above (stage4) determines Vy.
- Minimum device sizes ( $W=2\mu m$ ,  $L=1\mu m$ ) are used for both MN7 and MP8 to reduce loading on Vy and Vz.

$$Id_7 = Id_8 = 0.5\mu nCox(\frac{W_7}{L_7})vov_7^2(1 + \lambda(Vz - Vss)) \quad (7)$$

$$\tau_Z = (\frac{1}{gm_8})(Cgs_8 + Cdb_8 + Cgd_{10} + Cgd_7(1 + \frac{1}{|A3|}) + Cdb_7) \quad (8)$$

### Stage 2


- Vy from stage Z above determines the required ratio of R3 and R4.

$$(\frac{R4}{R3}) = \frac{Vss}{Vy} - 1 \quad (9)$$

- Gain of stage Y (Cascode amplifier) is set to 3.

$$|A2| = gm_4(R3 || R4) \quad (10)$$

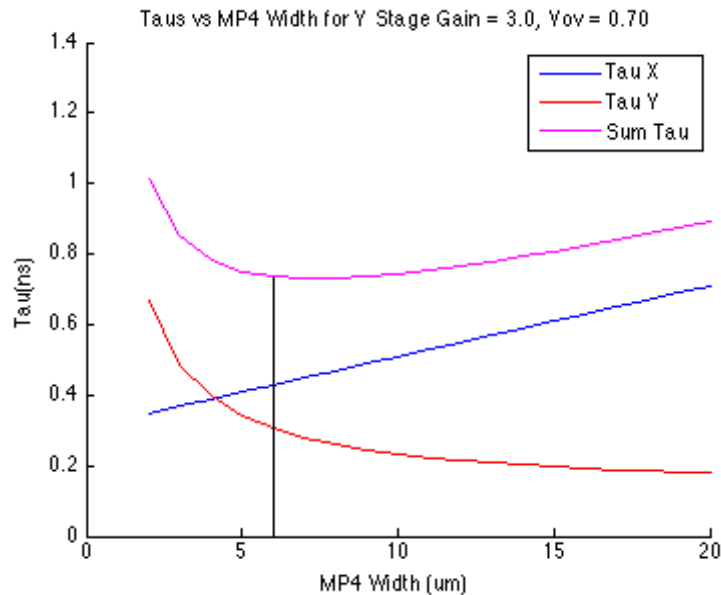- $Vov_4$  and  $W_4$  are optimized to reduce  $\tau_X$ .



- MN6 is sized such that current through MN6 is same as the current through MP4 and MP5.

$$Id4 = Id5 = Id6 = 0.5\mu pCox(\frac{W4}{L4})(Vdd - Vx - abs(Vtp))^2(1 + \lambda(Vdd - Vw)) \quad (11)$$

- Current through R3 and R4

$$I_{R3} + I_{R4} = V_{ss}/(R3 + R4) \quad (12)$$

$$\tau_Y = (R3||R4)(Cgs_7 + Cgd_7(1 + |A3|) + Cgd_6 + Cdb_6 + Cgd_5 + Cdb_5) \quad (13)$$

### Stage 1

- $V_{ov4}$  from stage 2 sets  $V_X$  which in turn sets the ratio of R1 and R2.

$$V_{ov4} = Vdd - Vx - |Vtp| \quad (14)$$

$$(\frac{R1}{R2}) = \frac{Vdd}{Vx} - 1 \quad (15)$$


- Gain of stage 1 (Common gate amplifier) is set to 10000.

$$|A1| = (R1||R2) \quad (16)$$

- MN1 and MP3 are sized such that  $Id1 = Id3$ .
- MN2 is sized to reduce  $\tau_{IIN}$  node.  $\tau_{IIN}$  is inversely proportional to  $gm_2$ .

$$\tau_{IIN} = (\frac{1}{gm_2})(Cin + Cgd_1 + Cdb_1 + Cgs_2 + Csb_2) \quad (17)$$

$$\tau_X = (R1||R2)(Cgd_2 + Cdb_2 + Cgd_3 + Cdb_3 + Cgs_4 + Cgd_4) \quad (18)$$

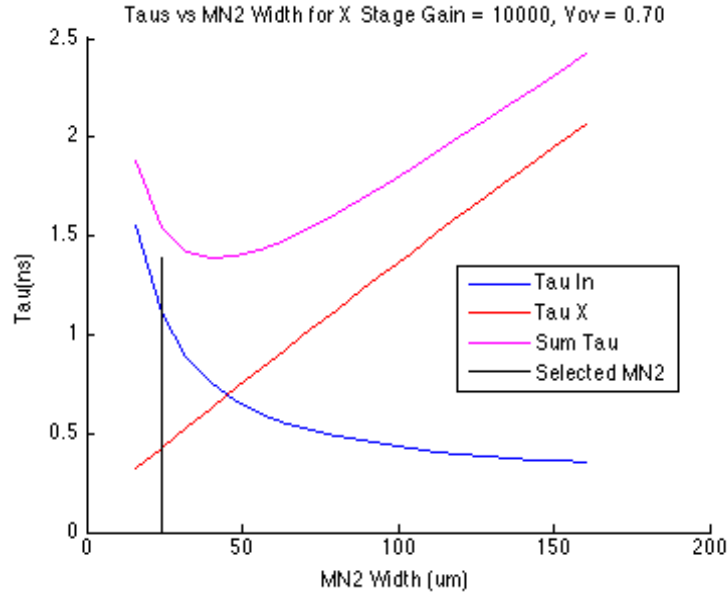

- Current through MN1, MN2 and MP3

$$Id_{1,2,3} = 0.5\mu pCox(\frac{W_3}{L_3})(Vdd - VbiasP - |Vtp|)^2(1 + \lambda(Vdd - Vx)) \quad (19)$$

- Current through R1 and R2

$$I_{R1} + I_{R2} = Vdd/(R1 + R2) \quad (20)$$

## Vovn, Vovp

- Vovn and Vovp are chosen to achieve a reasonable balance between gain, Tau total and Power, and our choice was educated by the gm/Id technology plots.

## Total Design Performance



$$|A_{TOTAL}| = A1 * A2 * A3 * A4 \quad (21)$$

$$\tau_{TOTAL} = \tau_{IN} + \tau_X + \tau_Y + \tau_Z + \tau_{OUTPUT} \quad (22)$$

$$Power = (V_{dd} - V_{ss})(I_{d1} + I_{d4} + I_{d7} + I_{d10}) + \left(\frac{V_{dd}^2}{R1 + R2}\right) + \left(\frac{V_{ss}^2}{R3 + R4}\right) \quad (23)$$


Bias Generator	Hand calc	Spice	%Error	Reason for error
$V_{BiasN}$	-1.300V	-1.279V	-1.6%	Startup circuit bias
$V_{BiasP}$	1.300V	1.319V	1.5%	Startup circuit bias
Stage1	Hand calc	Spice	%Error	Reason for error
$I_{d1}$	18.3 $\mu$ A	20.9 $\mu$ A	14.2%	Bias generator error
$V_X$	1.300V	1.275V	-1.9%	
$A_X$	10k $\Omega$	9.86k $\Omega$	-1.4%	Finite $MN_1$ and $MP_3$ output resistance
$gm_2$	210 $\mu$ S	268 $\mu$ S	27.6%	Bias generator error
$\tau_{IN}$	1.11ns			
$\tau_X$	420ps			
Stage2	Hand calc	Spice	%Error	Reason for error
$I_{d4}$	36.75 $\mu$ A	43.5 $\mu$ A	18.4%	
$V_W$	1.496V	1.450V	-3.2%	
$V_Y$	-1.550V	-1.418V	-8.5%	Imbalance between $MP_4$ and $MN_6$ current
$gm_4$	105 $\mu$ S	120 $\mu$ S	14.3%	Error in $V_Y$
$A_Y$	-3.0	-3.25	8.3%	Error estimating $gm_4$
$\tau_Y$	306ps			
Stage3	Hand calc	Spice	%Error	Reason for error
$I_{d7}$	10.25 $\mu$ A	22.9 $\mu$ A	123%	Error in $V_Y$ plus finite output resistance
$V_Z$	1.364	1.102V	-19.2%	Error in $V_Y$
$gm_7$	45 $\mu$ S	79 $\mu$ S	75.5%	Error in $I_{d7}$
$gm_8$	31.2 $\mu$ S	51 $\mu$ S	63.5%	Error in $I_{d7}$
$A_Z$	1.414	1.440	1.8%	The benefit of ratiometric design
$\tau_Z$	1.92ns			Error in estimating $gm_8$
Stage4	Hand calc	Spice	%Error	Reason for error
$I_{d10}$	2.96 $\mu$ A	30.43 $\mu$ A	928%	$MN_{10}$ 's large width is a big error amplifier
$V_{OUT}$	0.299	-0.117V	-139%	
$V_{t10}$	0.999	1.034V	3.5%	
$gm_{10}$	91.1 $\mu$ S	327 $\mu$ S	258%	
$gmb_{10}$	13.0 $\mu$ S	55.1 $\mu$ S	323%	
$A_{OUT}$	0.71	0.75	5.6%	
$\tau_{OUT}$	1.63ns			Error in estimating $gm_{10}$
Total Power	578 $\mu$ W	1.065mW	84%	Not accounting for bias gen
Total Gain	30.04k $\Omega$	34.66k $\Omega$	15.5%	Error in estimating gm

## 4 Simulated Bode Plots

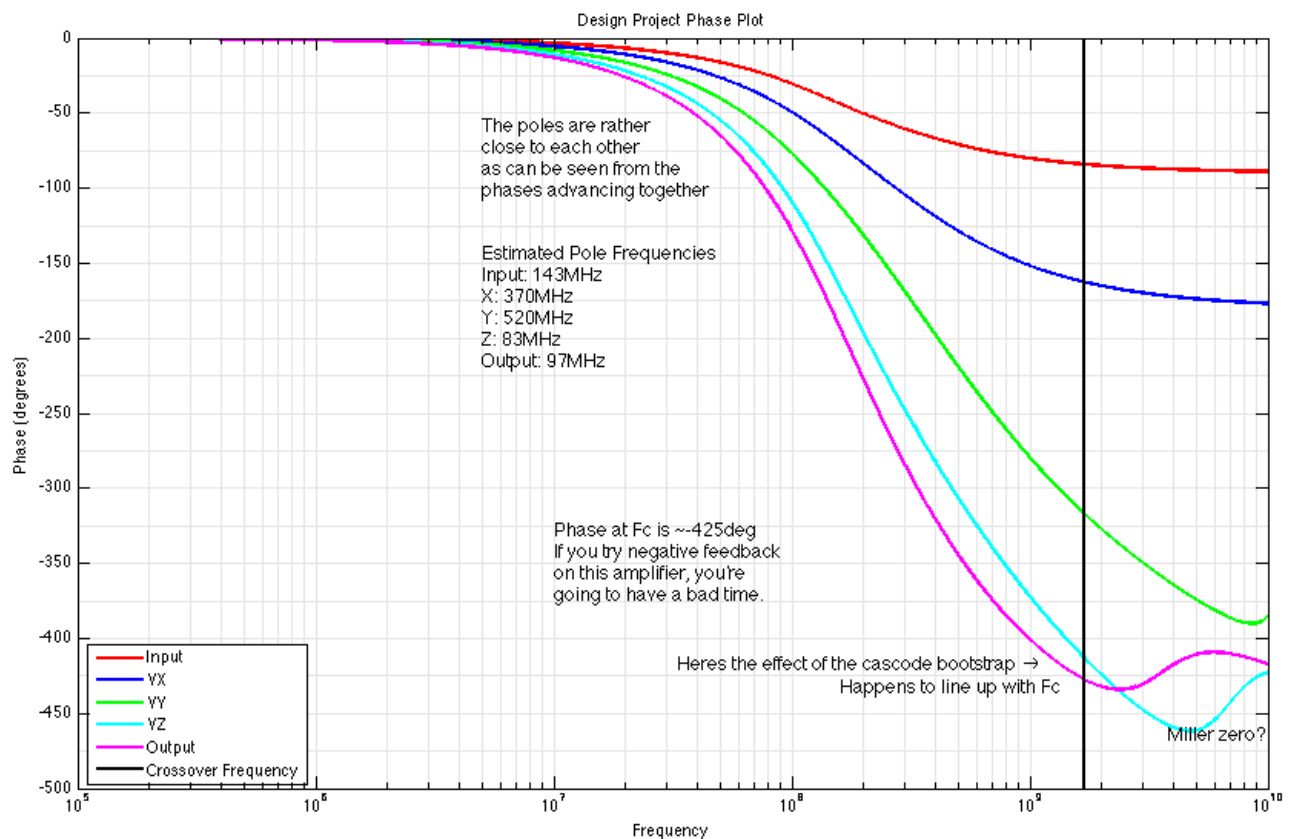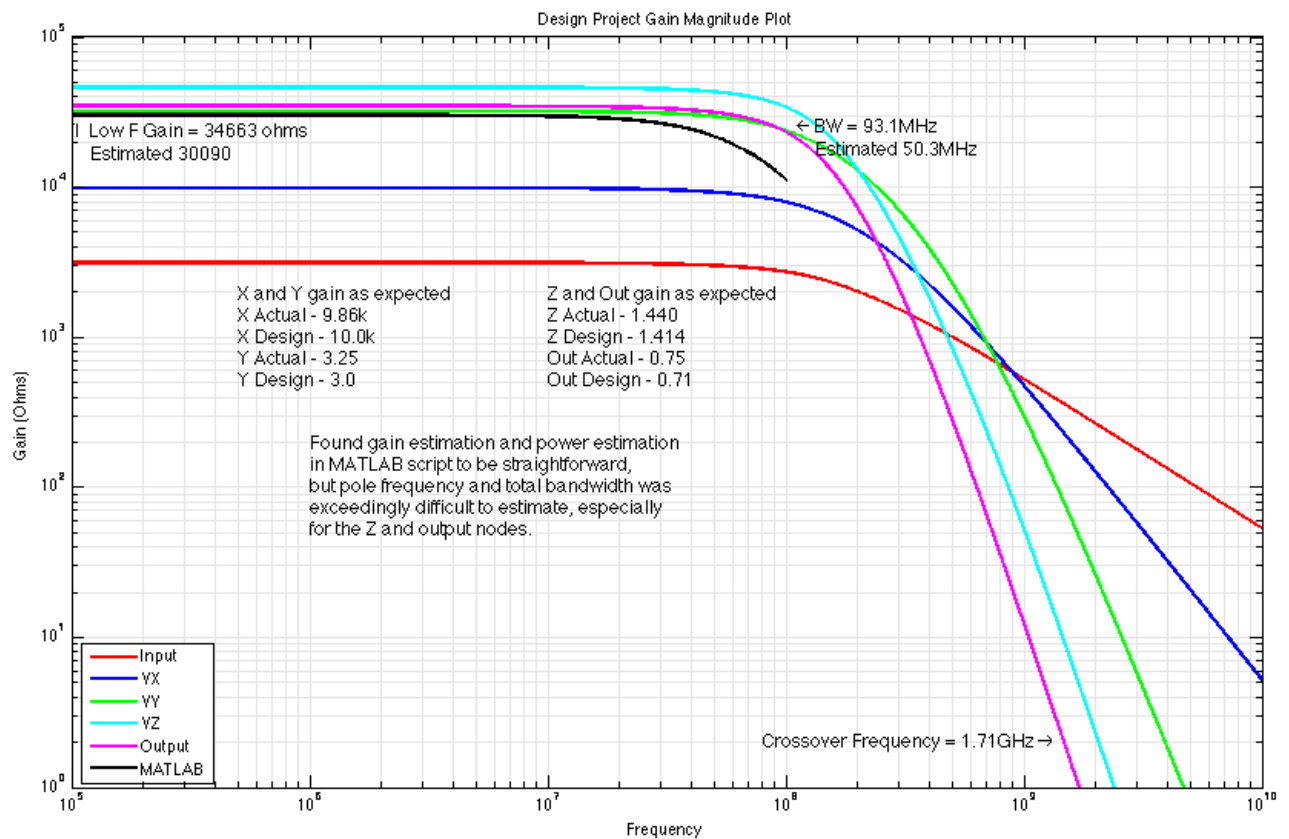



## 5 Simulated Transient Response

 

## 6 Comments and Conclusion

### 6.1 Notes about Design

- Resistors contribute to a large part of the overall gain. From manufacturability perspective, passive components are not friendly and also occupy more area on the chip. We feel that while the large value resistors helped us achieve a high gain and low power that they result in a possibly overly academic design that is not suitable for actual production.
- The output source follower stage is very sensitive to biasing due to back gate effect. Small variations on  $V_Z$  can drive the output to fall out of desired common mode voltage or drive  $MN_{10}$  into cutoff region and lose all the gain from previous stages.
- Any variations in supply voltage causes variation in  $V_{ov}$  of  $MN_7$  directly (as the device is biased through  $R_3$  &  $R_4$ ) causing  $V_Z$  to vary and thereby impacting the biasing of  $MN_{10}$  and gain. This is a great node to lose any and all PSRR.
- Common source stage with diode connected load attributes to miller cap loading effect on cascade stage. This is limiting the gain of common source stage to smaller values.
- Since the output is single ended, it is susceptible to noise, a differential configuration will be better.

### 6.2 Notes on Project

- We found it very difficult to balance the many simultaneous requirements, and I felt that this was a very useful exercise that's directly applicable to industry, and not only to chip design. Many times I have found myself trying to explore design spaces that have myriad of opposing non-orthogonal requirements. I feel like I have learned interesting ways to approach these problems both mathematically and strategically.

# 7 Appendix I

## 7.1 SPICE Netlist

```
1 | * Design Problem, ee114/214A-2015
2 | * Team Member 1 Name: Usha Kankanala
3 | * Team Member 2 Name: Samuel Lenius
4 | * Please fill in the specification achieved by your circuit
5 | * before you submit the netlist
6 | *****
7 | * sunetids of team members:
8 | *   ukankana@stanford.edu: 06091239
9 | *   lenius@stanford.edu:   06091240
10 | * The specification that this script achieves are:
11 | * Power          1.06mW      <= 2.00 mW      Meets Spec
12 | * Gain           34.6k0hm    >= 30.0 k0hm     Meets Spec
13 | * BandWidth      93.0MHz     >= 90.0 MHz      Meets Spec
14 | * FOM            3043        >= 1350         Meets Spec
15 | *****
16 |
17 | * Including the model file
18 | .include /usr/class/ee114/hspice/ee114_hspice.sp
19 |
20 |
21 | * Defining Top level circuit parameters
22 | .param p_Cin = 220f
23 | .param p_CL  = 250f
24 | .param p_RL  = 20k
25 |
26 | * Defining the supply voltages
27 | vdd      n_vdd  0      2.5
28 | vss      n_vss  0      -2.5
29 |
30 | *Defining the input current source
31 | ** For ac simulation uncomment the following 2 lines**
32 | Iin      n_iin  0      ac      100n
33 | *Iin     n_iin  0      ac      1
34 |
35 | ** For transient simulation uncomment the following 2 lines**
36 | *Iin     n_iin  0      sin(0 0.5u 1e6)
37 |
38 | * Defining Input capacitance
39 | Cin      n_iin  0      'p_Cin'
40 |
41 | * Defining the load
42 | RL       n_vout 0      'p_RL'
43 | CL       n_vout 0      'p_CL'
44 |
45 | *** Your Trans-impedance Amplifier here ***
46 | ***      d      g      s      b      n/pmos114      w      l
47 |
48 | *** Vx/Iin = V(n_x) / Iin, use "n_x" as the node label for Vx ***
49 | MN1      n_iin  n_bias_n  n_vss  n_vss  nmos114 w=3.0u l=2.0u
50 | MN2      n_x    0          n_iin  n_vss  nmos114 w=28.0u l=1.0u
51 | MP3      n_x    n_bias_p  n_vdd  n_vdd  pmos114 w=6.0u l=2.0u
52 | R1       n_vdd  n_x      19200
53 | R2       n_x    0        20800
54 |
55 | *** Vy/Vx = V(n_y) / V(n_x), use "n_y" as the node label for Vy ***
56 | MP4      n_w    n_x      n_vdd  n_vdd  pmos114 w=6.0u l=1.0u
57 | MP5      n_y    0        n_w    n_vdd  pmos114 w=6.0u l=1.0u
58 | MN6      n_y    n_bias_n  n_vss  n_vss  nmos114 w=3.0u l=2.0u
59 | R3       n_y    0        168100
```

```

60 R4      n_y      n_vss      34400
61
62 *** Vz/Vy = V(n_z) / V(n_y), use "n_z" as the node label for Vz ***
63 MN7     n_z      n_y      n_vss  n_vss  nmos114 w=2.0u l=1.0u
64 MP8     n_z      n_z      n_vdd  n_vdd  pmos114 w=2.0u l=1.0u
65
66 *** Vout/Vz = V(n_vout) / V(n_z), use "n_vout" as the node label for Vout ***
67 MN9     n_vout   n_bias_n  n_vss  n_vss  nmos114 w=5.0u l=2.0u
68 MN10    n_vdd    n_z      n_vout  n_vss  nmos114 w=28.0u l=1.0u
69
70 *** Your Bias Circuitry goes here ***
71 MP100   n_bias_n n_bias_p  n_vdd  n_vdd  pmos114 w=4u  l=2u
72 MP200   n_bias_p n_bias_p  n_vdd  n_vdd  pmos114 w=4u  l=2u
73 MN300   n_bias_n n_bias_n  n_vss  n_vss  nmos114 w=2u  l=2u
74 MN400   n_bias_p n_bias_n  n_biasr2 n_vss  nmos114 w=4u  l=2u
75 R200    n_biasr2 n_vss    16.7k
76 MP800   n_biasn9 n_bias_n  n_vdd  n_vdd  pmos114 w=2u  l=9u
77 MN700   n_biasn9 n_bias_n  n_vss  n_vss  nmos114 w=5u  l=2u
78 MN900   n_bias_p n_biasn9 n_vss  n_vss  nmos114 w=4u  l=2u
79
80 *** defining the analysis ***
81 .op
82 .option post brief nomod
83
84 ** For ac simulation uncomment the following line**
85 .ac dec 1k 100 1g
86
87 .measure ac gainmax_vout max vdb(n_vout)
88 .measure ac f3db_vout when vdb(n_vout)='gainmax_vout-3'
89
90 .measure ac gainmax_vx max vdb(n_x)
91 .measure ac f3db_vx when vdb(n_x)='gainmax_vx-3'
92
93 .measure ac gainmax_vy max vdb(n_y)
94 .measure ac f3db_vy when vdb(n_y)='gainmax_vy-3'
95
96 .measure ac gainmax_vz max vdb(n_z)
97 .measure ac f3db_vz when vdb(n_z)='gainmax_vz-3'
98
99 ** For transient simulation uncomment the following line **
100 *.tran 0.01u 4u
101
102 .end

```

## 7.2 SPICE .op Output

```

1  ***** HSPICE -- I-2013.12-SP2 64-BIT (May 27 2014) RHEL64 *****
2  Copyright (C) 2014 Synopsys, Inc. All Rights Reserved.
3  Unpublished-rights reserved under US copyright laws.
4  This program is protected by law and is subject to the
5  terms and conditions of the license agreement from Synopsys.
6  Use of this program is your acceptance to be bound by the
7  license agreement. HSPICE is the trademark of Synopsys, Inc.
8  Input File: Final_Samuel_Lenius_Usha_Kankanala_1p0_34p6_93p0_3043.sp
9  Command line options: Final_Samuel_Lenius_Usha_Kankanala_1p0_34p6_93p0_3043.sp
10 lic:
11 lic: FLEXlm: v10.9.8
12 lic: USER:      lenius          HOSTNAME: corn27.stanford.edu
13 lic: HOSTID: 001b213a6bad      PID:      6922
14 lic: Using FLEXlm license file:
15 lic: 27000@cadlic0
16 lic: Checkout 1 hspice
17 lic: License/Maintenance for hspice will expire on 09-jan-2016/2015.06
18 lic: 1(in_use)/200(total) FLOATING license(s) on SERVER 27000@cadlic0

```

```

19  lic:
20
21
22  *****
23  ***** option summary
24  *****
25  runlvl = 3          bypass = 2
26  **info** dc convergence successful at Newton-Raphson method
27  ***** HSPICE -- I-2013.12-SP2 64-BIT (May 27 2014) RHEL64 *****
28  *****
29  * design problem, ee114/214a-2015
30
31  ***** operating point information tnom= 25.000 temp= 25.000 *****
32  ***** operating point status is all simulation time is 0.
33      node      =voltage      node      =voltage      node      =voltage
34
35  +0:n_bias_n=  -1.2795  0:n_bias_p=   1.3194  0:n_biasn9=  -1.9549
36  +0:n_biasr2=  -2.2972  0:n_iin   =  -1.0243  0:n_vdd    =   2.5000
37  +0:n_vout   = -117.4867m 0:n_vss   =  -2.5000  0:n_w     =   1.4507
38  +0:n_x      =   1.2754  0:n_y     =  -1.4186  0:n_z     =   1.1019
39
40
41  **** voltage sources
42
43  subckt
44  element  0:vdd      0:vss
45  volts    2.5000    -2.5000
46  current  -236.5422u 189.5402u
47  power    591.3555u 473.8505u
48
49      total voltage source power dissipation=   1.0652m      watts
50
51
52
53  **** current sources
54
55  subckt
56  element  0:iin
57  volts    -1.0243
58  current   0.
59  power     0.
60
61
62      total current source power dissipation=   0.      watts
63
64  **** resistors
65
66  subckt
67  element  0:r1      0:r1      0:r2      0:r3      0:r4      0:r200
68  r value  20.0000k  19.2000k  20.8000k  168.1000k  34.4000k  16.7000k
69  v drop   -117.4867m 1.2246   1.2754   -1.4186   1.0814   202.7945m
70  current  -5.8743u  63.7831u 61.3156u -8.4393u  31.4349u 12.1434u
71  power    690.1559n 78.1111u 78.1997u 11.9723u 33.9924u 2.4626u
72
73
74
75  **** mosfets
76
77
78  subckt
79  element  0:mn1      0:mn2      0:mp3      0:mp4      0:mp5      0:mn6
80  model    0:nmos114. 0:nmos114. 0:pmos114. 0:pmos114. 0:pmos114. 0:nmos114.
81  region   Saturati  Saturati  Saturati  Saturati  Saturati  Saturati
82  id       20.9028u  20.9028u -18.4353u -43.5146u -43.5146u 20.5190u

```

83	ibs	0.	-14.7571f	0.	0.	10.4928f	0.
84	ibd	-14.7571f	-37.7536f	12.2464f	10.4928f	39.1864f	-10.8136f
85	vgs	1.2205	1.0243	-1.1806	-1.2246	-1.4507	1.2205
86	vds	1.4757	2.2997	-1.2246	-1.0493	-2.8694	1.0814
87	vbs	0.	-1.4757	0.	0.	1.0493	0.
88	vth	500.0000m	868.4718m	-500.0000m	-500.0000m	-779.2740m	500.0000m
89	vdsat	720.4904m	155.8143m	-680.6195m	-724.6359m	-671.4420m	720.4904m
90	vod	720.4904m	155.8143m	-680.6195m	-724.6359m	-671.4420m	720.4904m
91	beta	80.5339u	1.7220m	79.5924u	165.7393u	193.0403u	79.0551u
92	gam eff	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m
93	gm	58.0239u	268.3046u	54.1721u	120.1006u	129.6154u	56.9584u
94	gds	973.3246n	1.6995u	868.5804n	3.9382u	3.3813u	973.3246n
95	gmb	19.4618u	53.3569u	18.1699u	40.2830u	28.5941u	19.1044u
96	cdtot	5.3930f	27.9761f	9.8099f	10.0272f	7.8875f	5.6372f
97	cgtot	12.3208f	72.3462f	24.6430f	15.3124f	15.3250f	12.3136f
98	cstot	16.1000f	74.6671f	31.0001f	21.8000f	19.2080f	16.1000f
99	cbtot	9.3595f	32.7274f	16.5627f	16.7010f	11.9148f	9.6109f
100	cgs	10.7000f	56.9335f	21.4001f	12.2000f	12.2000f	10.7000f
101	cgd	1.5272f	14.1975f	3.0451f	3.0193f	3.0528f	1.5199f
102							
103							
104							
105	subckt						
106	element	0:mn7	0:mp8	0:mn9	0:mn10	0:mp100	0:mp200
107	model	0:nmos114.	0:pmos114.	0:nmos114.	0:nmos114.	0:pmos114.	0:pmos114.
108	region	Saturati	Saturati	Saturati	Saturati	Saturati	Saturati
109	id	22.9857u	-22.9857u	36.3091u	30.4348u	-13.7696u	-12.2647u
110	ibs	0.	0.	0.	-23.8251f	0.	0.
111	ibd	-36.0186f	13.9814f	-23.8251f	-50.0000f	37.7951f	11.8062f
112	vgs	1.0814	-1.3981	1.2205	1.2194	-1.1806	-1.1806
113	vds	3.6019	-1.3981	2.3825	2.6175	-3.7795	-1.1806
114	vbs	0.	0.	0.	-2.3825	0.	0.
115	vth	500.0000m	-500.0000m	500.0000m	1.0337	-500.0000m	-500.0000m
116	vdsat	581.3598m	-898.1364m	720.4904m	185.6306m	-680.6195m	-680.6195m
117	vod	581.3598m	-898.1364m	720.4904m	185.6306m	-680.6195m	-680.6195m
118	beta	136.0186u	56.9907u	139.8907u	1.7664m	59.4488u	52.9515u
119	gam eff	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m
120	gm	79.0758u	51.1854u	100.7899u	327.9067u	40.4620u	36.0399u
121	gds	1.6899u	2.0166u	1.6222u	2.4121u	579.0536n	579.0536n
122	gmb	26.5228u	17.1681u	33.8060u	55.1425u	13.5714u	12.0881u
123	cdtot	3.6813f	4.2306f	7.0089f	26.8604f	5.7669f	7.1139f
124	cgtot	5.1272f	5.1004f	20.5625f	72.0600f	16.4914f	16.4276f
125	cstot	8.6667f	8.6667f	24.8334f	72.6537f	21.3667f	21.3667f
126	cbtot	7.2976f	7.8472f	11.5918f	29.2575f	10.9061f	12.3169f
127	cgs	4.0667f	4.0667f	17.8334f	56.9335f	14.2667f	14.2667f
128	cgd	1.0221f	1.0086f	2.5731f	14.2248f	2.0927f	2.0290f
129							
130							
131							
132	subckt						
133	element	0:mn300	0:mn400	0:mp800	0:mn700	0:mn900	
134	model	0:nmos114.	0:nmos114.	0:pmos114.	0:nmos114.	0:nmos114.	
135	region	Saturati	Saturati	Saturati	Linear	Saturati	
136	id	13.7696u	12.1434u	-31.3543u	31.3543u	121.3242n	
137	ibs	0.	-2.0279f	0.	0.	0.	
138	ibd	-12.2049f	-38.1938f	44.5486f	-5.4514f	-38.1938f	
139	vgs	1.2205	1.0177	-3.7795	1.2205	545.1376m	
140	vds	1.2205	3.6166	-4.4549	545.1376m	3.8194	
141	vbs	0.	-202.7945m	0.	0.	0.	
142	vth	500.0000m	564.1814m	-500.0000m	500.0000m	500.0000m	
143	vdsat	720.4904m	453.5145m	-3.2795	545.1376m	45.1376m	
144	vod	720.4904m	453.5145m	-3.2795	720.4904m	45.1376m	
145	beta	53.0512u	118.0829u	5.8305u	128.4071u	119.0969u	
146	gam eff	600.0000m	600.0000m	600.0000m	600.0000m	600.0000m	

```

147 gm      38.2229u   53.5523u   19.1213u   69.9995u   5.3757u
148 gds     648.8830n  514.1885n  331.9501n  24.0427u   5.0935n
149 gmb     12.8204u   16.0433u   6.4135u   23.4786u   1.8031u
150 cdtot    4.4573f    5.5601f    3.5781f   13.8464f   5.5651f
151 cgtot    8.2107f    16.5346f   29.9091f   25.3172f   17.7794f
152 cstot   11.7334f    20.0468f   33.2001f   24.2459f   20.4667f
153 cbtot    8.1048f    9.4306f    6.9952f   13.0872f   11.0903f
154 cgs      7.1334f    14.2667f   28.6001f   17.2459f   14.2667f
155 cgd      1.0150f    2.0887f    1.2459f    7.9152f    2.0937f
156
157
158
159 *****
160 * design problem, ee114/214a-2015
161
162 ***** ac analysis tnom= 25.000 temp= 25.000 *****
163 gainmax_vout= -49.2028      at= 5.3333k
164      from= 100.0000      to= 1.0000g
165 f3db_vout= 92.9703x
166 gainmax_vx= -60.1155      at= 36.1410k
167      from= 100.0000      to= 1.0000g
168 f3db_vx= 131.9439x
169 gainmax_vy= -49.8772      at= 21.4289k
170      from= 100.0000      to= 1.0000g
171 f3db_vy= 108.3150x
172 gainmax_vz= -46.7065      at= 21.3304k
173      from= 100.0000      to= 1.0000g
174 f3db_vz= 105.6056x
175
176 ***** job concluded
177 ***** HSPICE -- I-2013.12-SP2 64-BIT (May 27 2014) RHEL64 *****
178 *****
179 * design problem, ee114/214a-2015
180
181 ***** job statistics summary tnom= 25.000 temp= 25.000 *****
182
183
184 ***** Machine Information *****
185 CPU:
186 model name      : Quad-Core AMD Opteron(tm) Processor 2384
187 cpu MHz         : 2700.000
188
189 OS:
190 Linux version 3.13.0-53-generic (buildd@phianna) (gcc version 4.8.2 (Ubuntu
    4.8.2-19ubuntu1) ) #89-Ubuntu SMP Wed May 20 10:34:39 UTC 2015
191
192
193 ***** HSPICE Threads Information *****
194
195 Command Line Threads Count : 1
196 Available CPU Count        : 8
197 Actual Threads Count       : 1
198
199
200 ***** Circuit Statistics *****
201 # nodes      = 13 # elements = 28
202 # resistors  = 6 # capacitors = 2 # inductors = 0
203 # mutual_inds = 0 # vccs = 0 # vcvs = 0
204 # cccs = 0 # ccvs = 0 # volt_srcs = 2
205 # curr_srcs = 1 # diodes = 0 # bjts = 0
206 # jfets = 0 # mosfets = 17 # U elements = 0
207 # T elements = 0 # W elements = 0 # B elements = 0
208 # S elements = 0 # P elements = 0 # va device = 0
209 # vector_srcs = 0 # N elements = 0

```


```

210
211
212 ***** Runtime Statistics (seconds) *****
213
214 analysis          time      # points   tot. iter  conv.iter
215 op point          0.00           1         10
216 ac analysis       0.08        7001       7001
217 readin            0.01
218 errchk            0.00
219 setup             0.00
220 output            0.01
221
222
223          peak memory used          176.94 megabytes
224          total cpu time              0.10 seconds
225          total elapsed time          1.24 seconds
226          job started at      06:17:16 12/04/2015
227          job ended   at      06:17:17 12/04/2015
228
229
230 lic: Release hspice token(s)
231 lic: total license checkout elapse time:          1.04(s)

```



### 7.3 Amplifier - Enlarged

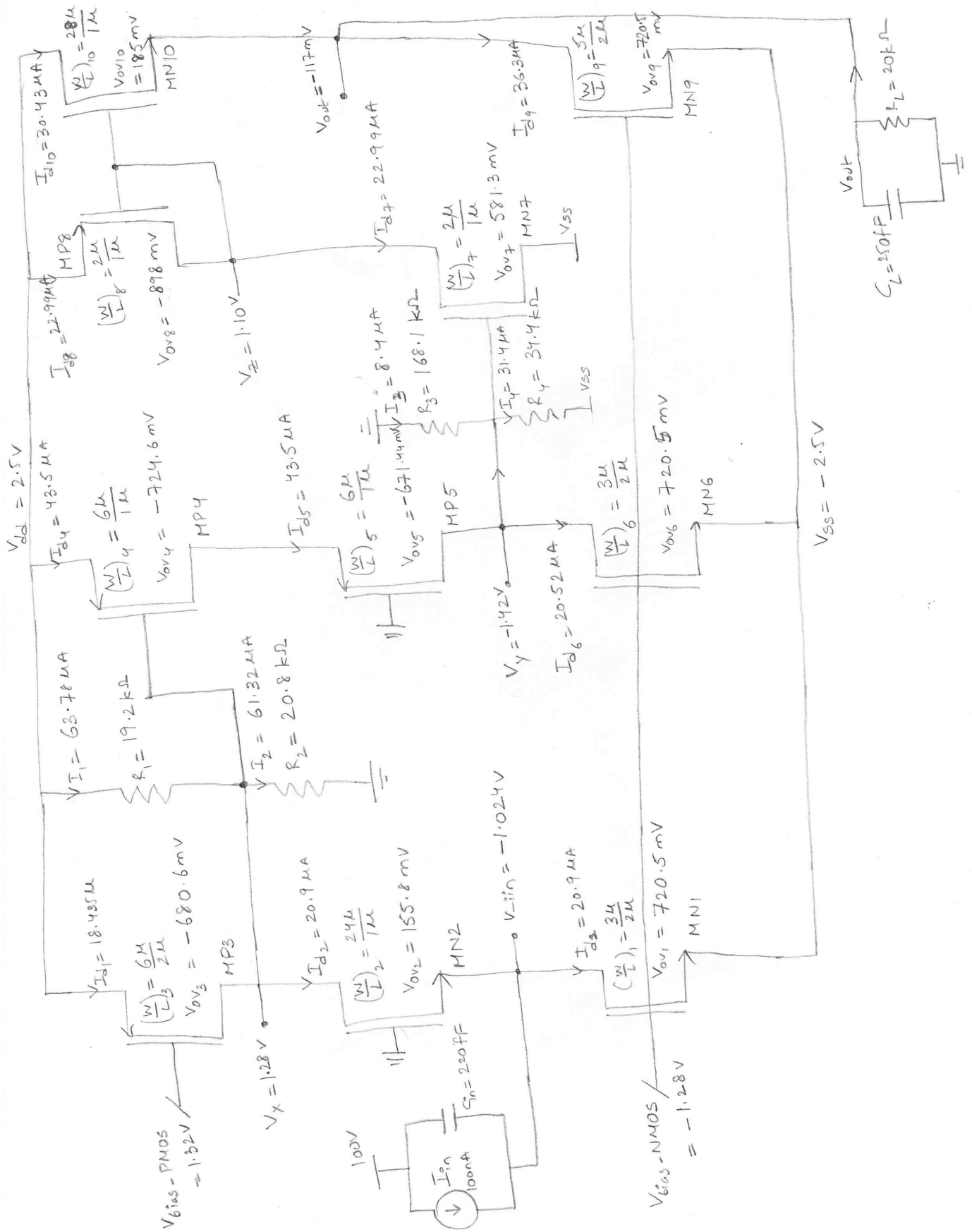

## 7.4 Bias Circuit - Enlarged

